

1

ASSIGNMENT - 4

Submitted by- Sec B
20210010027
Anushka Saxena

Date: 12/3/22

Q1 (a) Characteristic table

P	N	$Q(t+1)$
0	0	0
0	1	$\overline{Q(t)}$
1	0	$\overline{Q(t)}$
1	1	1

P	N	$Q(t)$	$Q(t+1)$
0	0	0	0 } 0
0	0	1	0 }
0	1	0	0 } P
0	1	1	1 } Q(t)
1	0	0	1 } Q(t)
1	0	1	0 }
1	1	0	1 } 1
1	1	1	1 }

Characteristic equation

$NQ(t)$			
00	01	11	10
0			1
1	1		1

~~Q(t+1) = NQ(t) + PQ(t)~~

$$\Rightarrow Q(t+1) = NQ(t) + P \overline{Q(t)}$$



Characteristic equation

④ Excitation table:

$Q(t)$	P	N	$Q(t+1)$
0	0	x	0
0	1	x	1
1	x	0	0
1	x	1	1

(d) Excitation table with D: $D = Q(t+1)$


$Q(t)$	D	$Q(t+1)$	P	N
0	0	0	0	x
0	1	1	1	x
1	0	0	x	0
1	1	1	x	1

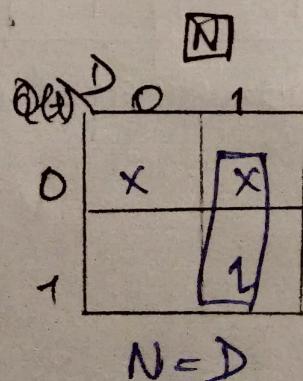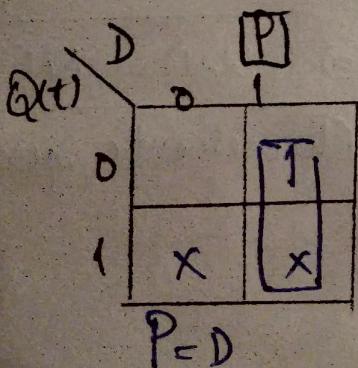

⇒ Connect both P and N to D

3

Q2

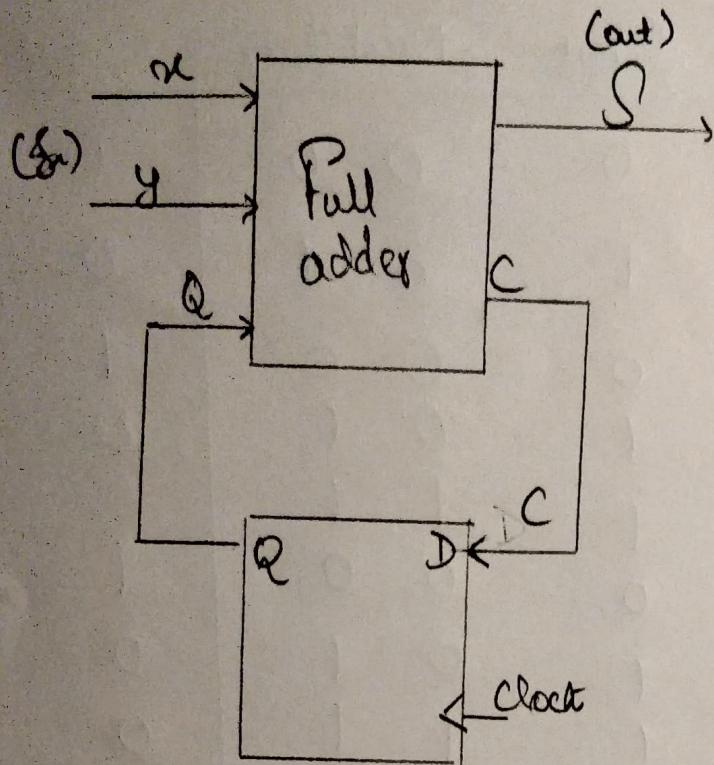

$$\underline{S = A \oplus B \oplus Q}$$

$$S = x \oplus y \oplus Q$$

$$C = xy + yQ + xQ$$


$$\text{Since } D = Q(t+1)$$

$$\begin{aligned} Q(t+1) &= D = xy + yQ + xQ \\ &\equiv C \end{aligned}$$

State table

Present $Q(t)$	Input x y	Next $Q(t+1)$	Output S
0	0 0	0	0
0	0 1	0	1
0	1 0	0	1
0	1 1	1	0
1	0 0	0	1
1	0 1	1	0
1	1 0	1	0
1	1 1	1	1

State diagram -

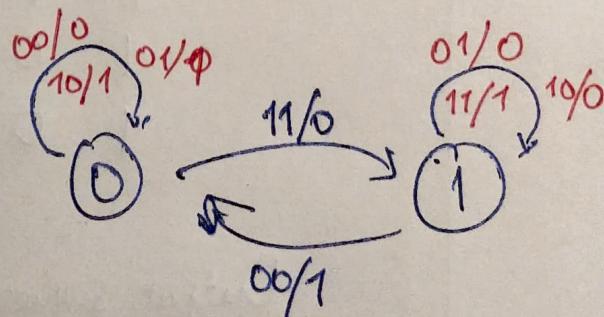

Q3 (a)

	Present State	Input	Next state	Output
	0 0	0	0 0	0
	0 0	1	0 1	0
	0 1	0	0 0	1
	0 0	1	0 1	0
	0 1	1	1 1	0
	1 1	0	0 0	1
	0 0	1	0 1	0
	0 1	1	1 1	0
	1 1	1	1 0	0
	1 0	0	0 0	1
	0 0	1	0 0	0
	0 1	1	1 1	0
	1 1	1	1 0	0
	1 0	1	1 0	0
	1 0	0	0 0	1


Output Sequence → 001001 0001 00001

5

Q3 (b)

Present state	Input	Next state	Output
a	0	f	0
f	1	b	1
b	1	c	0
c	1	e	0
e	0	d	0
d	0	g	1
g	1	h	1
h	0	g	1
g	0	g	0
g	1	h	1
h	1	ag	0

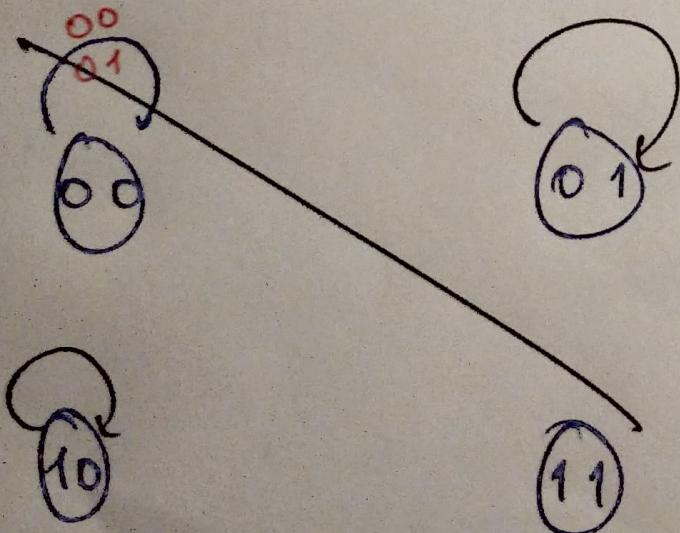Output sequence $\rightarrow 01000111010$



6

Q_4 $E=0$, Next State = Present State (No change)

$E=1, F=1 \Rightarrow$

Present Next
 $00 \rightarrow 01$
 $01 \rightarrow 10$
 $10 \rightarrow 11$
 $11 \rightarrow 00$

$E=1, F=0 \Rightarrow$

$00 \rightarrow 11$
 ~~$01 \rightarrow 01$~~
 $11 \rightarrow 10$
 $10 \rightarrow 01$
 $01 \rightarrow 00$

Present State		Input		Next State		Input to ff			
A	B	E	F	A ⁺	B ⁺	J _A	K _A	J _B	K _B
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

J_A

AB	EF	00	01	11	10
00					1
01				1	
11		X	X	X	X
10		X	X	X	X

$B\bar{E}F$ $\bar{B}EF$

K_A

AB	EF	00	01	11	10
00		X	X	X	X
01		X	X	X	X
11				1	
10					1

$B EF$ $\bar{B} E \bar{F}$

$$J_A = BEF + \bar{B}EF$$

$$= E(B \odot F)$$

$$K_A = BEF + \bar{B}E\bar{F}$$

$$= E(B \odot F)$$

J_B


AB	EF	00	01	11	10
00				1	1
01		X	X	X	X
11		X	X	X	X
10				1	1

$J_B = F$

K_B

AB	EF	00	01	11	10
00		X	X	X	X
01				1	1
11				1	1
10		X	X	X	X

$K_B = F$

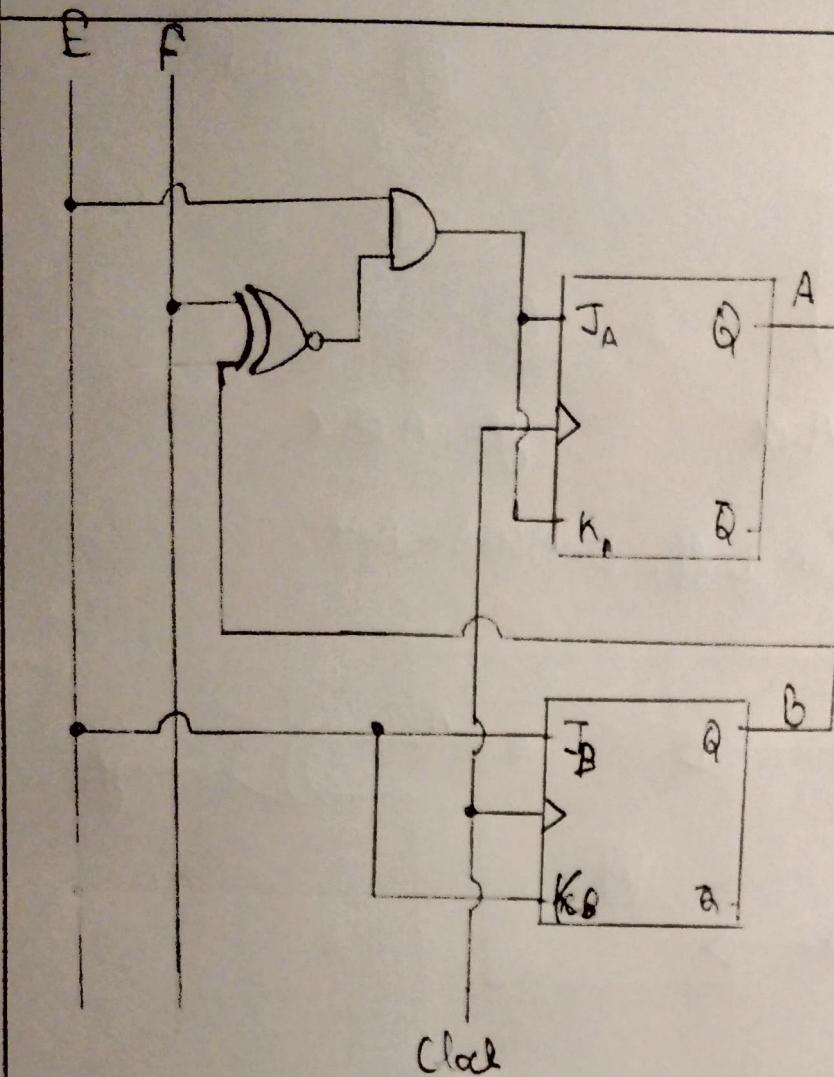

Q5 State table :

Present state $A(t)$	Input x	Next state $A(t+1)$	Output y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

9


	x	$A(t+1)$
A	0	0 1
	0	1 1
	1	1 1

	x	y	Output
A	0	0	1
	1	1	1


$$A(t+1) = A + x$$

$$y = A \oplus x$$

for D ff, $D = A(t+1) = A + x$

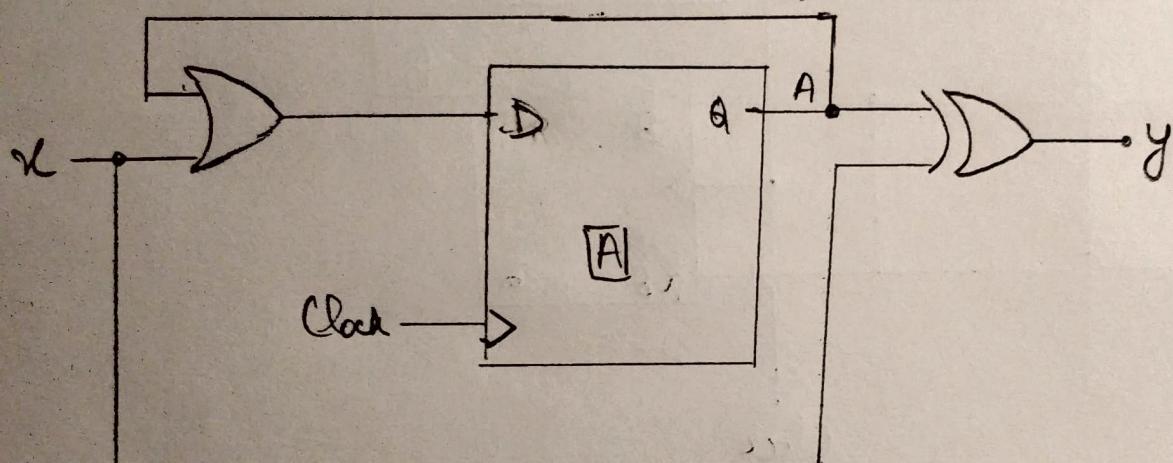

10

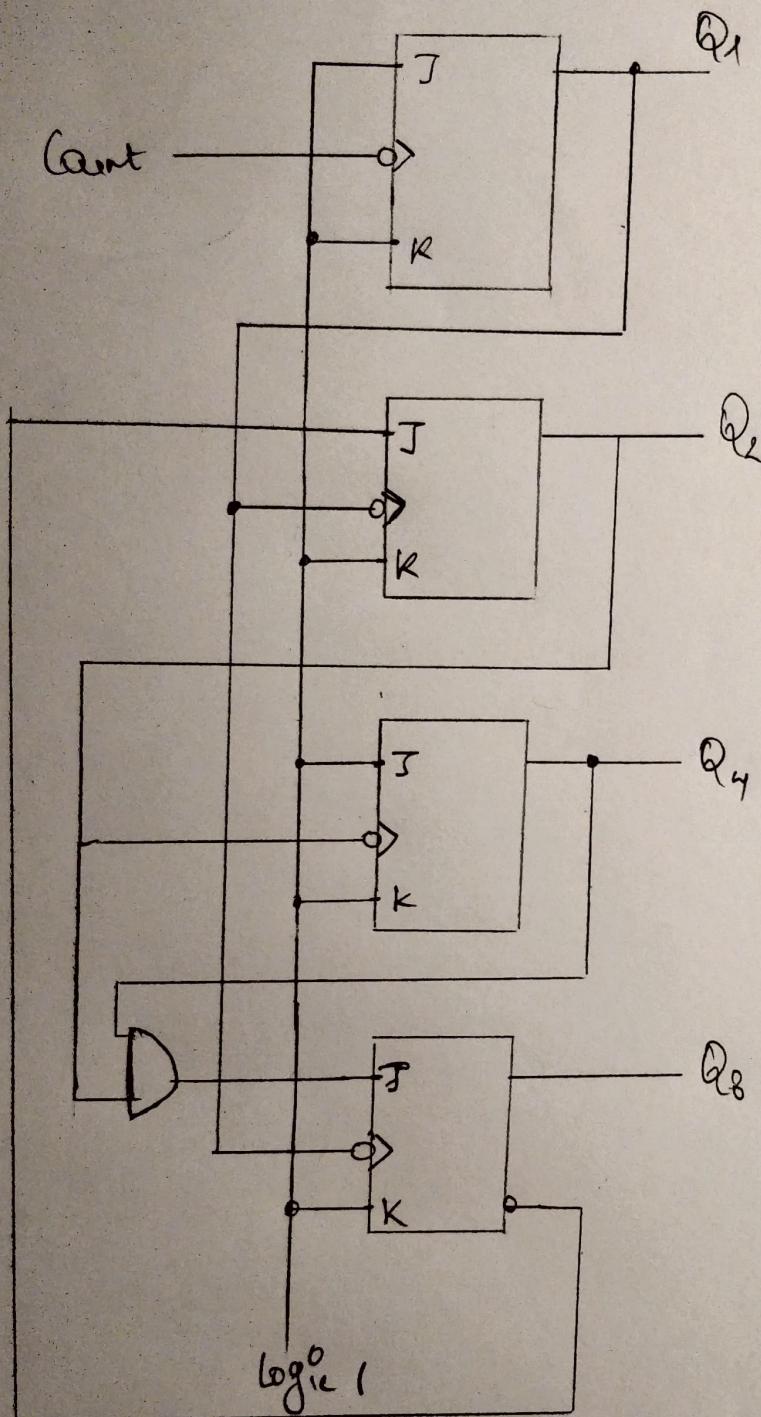Q_b

When noise signals result in any unused state, it goes to the next unused state and then resets to used values.

Unused	Next state	Next state
Q ₃ Q ₂ Q ₁		
1 0 1 0	1 0 1 1	0 1 0 0
1 1 0 0	1 1 0 1	0 1 0 0
1 1 1 0	1 1 1 1	0 0 0 0

Eg → Noise
1100
↓
1101
↓
0100