

Dtd: 17/12/21

Submitted (Section B) 1  
by →

Anushtan Saxena  
S20210010027


# EXPERIMENT 1

Using NAND, a universal gate, to build other gates.


(I) AIM → Make a NOT gate using NAND:

SOFTWARE USED → Logisim.

PROCEDURE →

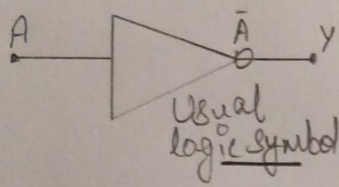

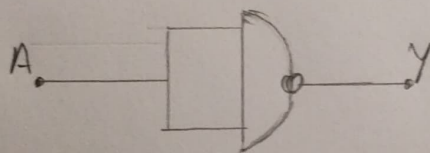Boolean expression  $\equiv Y = \bar{A}$   
for a NOT gate



NOT gate using NAND

Verification :-

case(i) → When  $A = 0$ ,  $Y = (\bar{A} * A) = (\bar{0} * 0) = 1$  which is correct.

case(ii) → When  $A = 1$ ,  $Y = (\bar{1} * 1) = 0$  which is also correct.

Truth table →

A	$Y = \bar{A}$
1	0
0	1


CONCLUSION → The easiest gate to produce, this NOT gate is simulated in logisim and is verified with the inputs shown in the truth table.



(II) AIM → Make an AND gate using NAND.


SOFTWARE USED → Logisim

PROCEDURE →

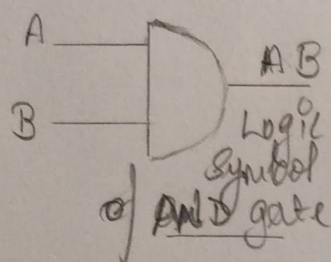

Boolean expression for AND gate  $\Rightarrow Y = AB$

→ AND gate using NAND →

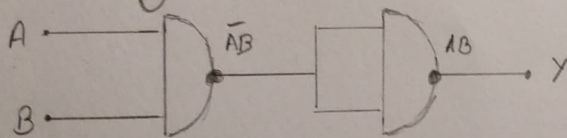

VERIFICATION:

case(i) → When  $A=0$ ,  $B=0$ ,  $Y = 0 \cdot 0 = 0$   
Verified through logisim.

case(ii) → When  $A=1$ ,  $B=1$ ,  
 $Y = 1 \cdot 1 = 1$   
Verified through logisim.

case(iii) → when  $A=0$ ,  $B=1$

$Y = 0 \cdot 1 = 0$   
Verified through logisim

Truth table →

A	B	Y
1	1	1
1	0	0
0	1	0
0	0	0


CONCLUSION → The AND gate produced is verified in  
logisim through simulation with the given truth table.



(III) AIM → Make an OR gate using NAND:


SOFTWARE USED → Logisim

PROCEDURE →

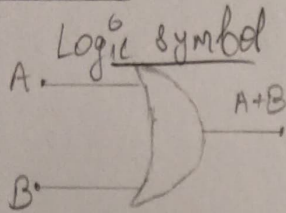

Boolean expression for OR gate  $\Rightarrow Y = A + B$

→ OR gate using NAND →

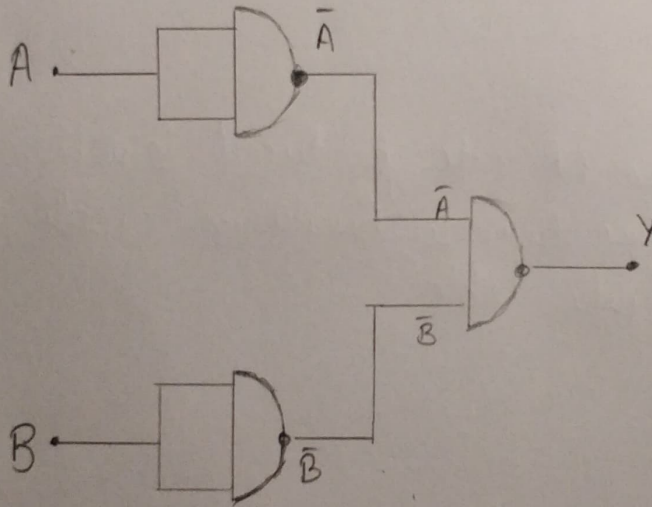

Verification →

Truth table:

A	B	Y
1	1	1
1	0	1
0	1	1
0	0	0



5

case (i)  $\rightarrow$  When  $A=0, B=0,$

$$Y = 0+0 = 0$$

which is verified through logisim.

case (ii)  $\rightarrow$  When  $A=1, B=0,$

$$Y = 1+0 = 1$$

verified through logisim.

case (iii)  $\rightarrow$  When  $A=1, B=1,$

$$Y = 1+1 = 1,$$

verified through logisim.


CONCLUSION  $\rightarrow$  The OR gate produced is verified in logisim through simulation with the given truth table.



(IV) AIM → Make a NOR gate using NAND :


SOFTWARE USED → Logisim.

PROCEDURE →

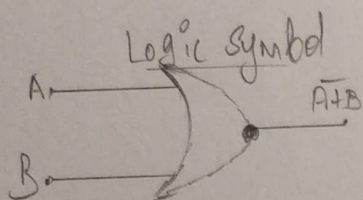

Boolean expression for NOR gate  $\Rightarrow Y = \overline{A+B}$

→ NOR gate using NAND →

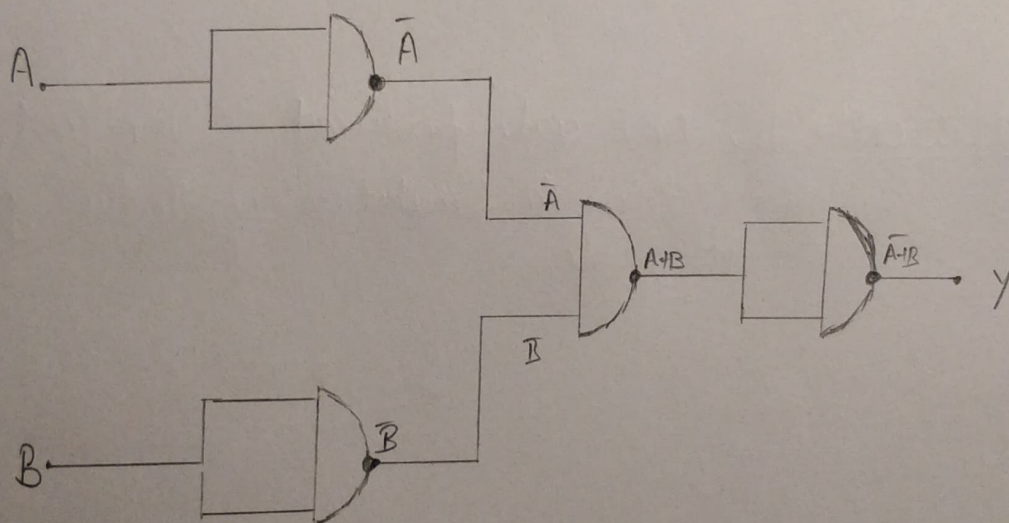

Verification :-

Truth table :

A	B	Y
1	1	0
1	0	0
0	1	0
0	0	1

Case (i)  $\rightarrow$  When  $A=0, B=0,$

$$Y = \overline{0+0} = 1$$

which is verified through logisim.

Case (ii)  $\rightarrow$  When  $A=1, B=0,$

$$Y = \overline{1+0} = 0,$$

verified through logisim.

Case (iii)  $\rightarrow$  When  $A=1, B=1,$

$$Y = \overline{1+1} = 0,$$

verified through logisim


CONCLUSION  $\rightarrow$  The NOR gate produced is verified in logisim through simulation with the given truth table.



(V) AIM → Make an XOR gate using NAND gate :


SOFTWARE USED → Logisim

PROCEDURE →

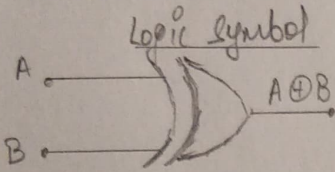

Boolean expression ⇒  $Y = A\bar{B} + \bar{A}B$   
for Xor gate  
 $= A \oplus B$

→ XOR gate using NAND →

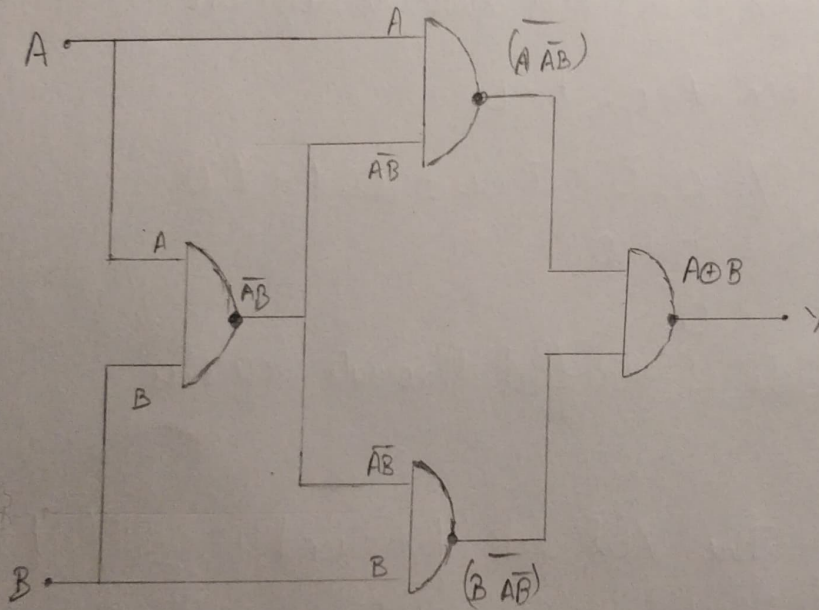

Verification →

Truth table :

A	B	Y
1	1	0
1	0	1
0	1	1
0	0	0



Case(i) → When  $A=1, B=1,$

$$Y = 1 \cdot \bar{1} + \bar{1} \cdot 1 = 1 \cdot 0 + 0 \cdot 1 \\ = 0 + 0 = 0$$

which is verified through logisim.

Case(ii) → When  $A=0, B=1,$

$$Y = 0 \cdot \bar{1} + \bar{0} \cdot 1 \\ = 0 + 1 = 1$$

which is verified through logisim.

Case(iii) → When  $A=0, B=0,$

$$Y = 0 \cdot \bar{0} + \bar{0} \cdot 0 = 0 \cdot 1 + 1 \cdot 0 \\ = 0 + 0 \\ = 0$$

which is verified through logisim.

CONCLUSION → The XOR gate produced is verified in logisim through simulation with the given truth table.