

# Experiment-1

NAME:-

Date:- 24-12-2020

Roll No:-


Aim:- To Verify XOR Gate Using NAND Gate.

Software used:-

1. Logisim software

Truth Table:-

Truth table for XOR Gate

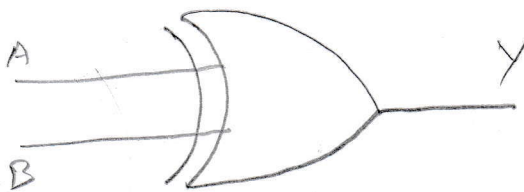


Logic Symbol

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Boolean Expression:-


Now by using K-map for Y

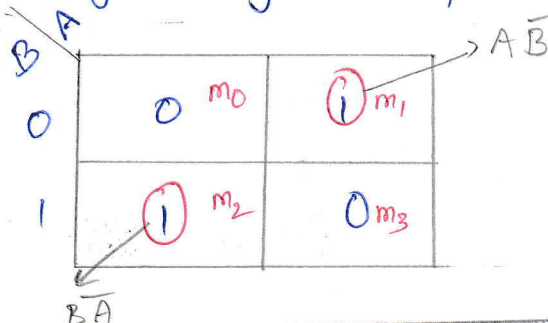

$$Y = A\bar{B} + \bar{A}B$$

$$Y = A \oplus B$$

### Logic Diagram:-

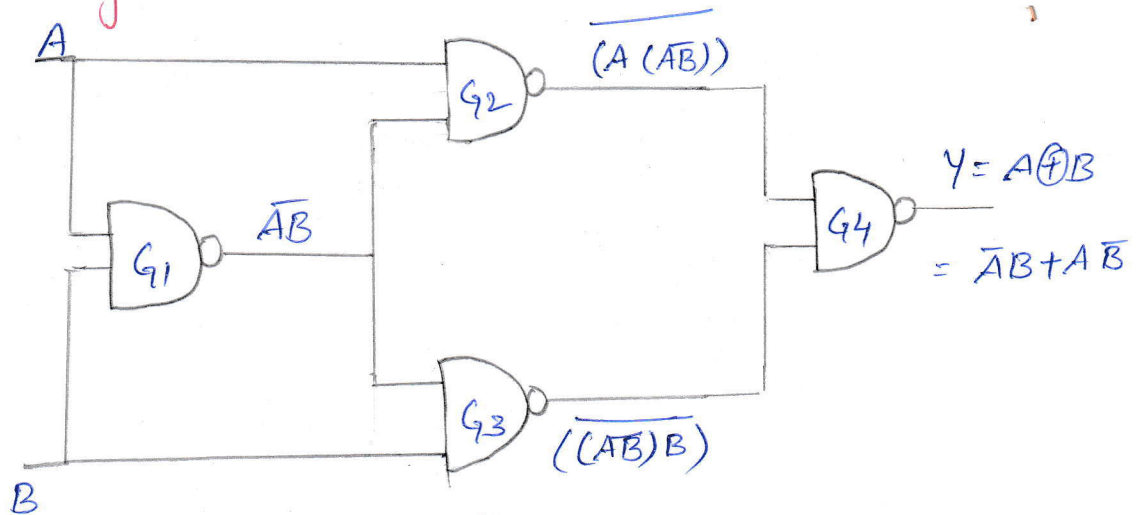

### Checking of the Circuit:

Case (i) If  $A = "0"$  and  $B = "0"$  then  $Y = "0"$

by substituting in equation "y"

$$\begin{aligned} Y &= \overline{AB} + A\overline{B} \\ &= \overline{0 \cdot 0} + 0 \cdot \overline{0} \\ &= \overline{0 \cdot 0} + 0 \cdot 1 \\ &= 1 \end{aligned}$$

Case (ii) If  $A = "0"$  and  $B = "1"$  then  $Y = "1"$

by substituting in equation "y"

$$\begin{aligned} Y &= \overline{AB} + A\overline{B} \\ &= \overline{0 \cdot 1} + 0 \cdot \overline{1} \\ &= \overline{0 \cdot 1} + 0 \cdot 0 \\ &= 1 \end{aligned}$$

**Conclusion:** The XOR Gate using Nand circuit is simulated in logisim and is Verified with the inputs, shown in the truth table.