

Dated: 21/1/22

Submitted by-

Anushthan Saxena
G20210010027

ASSIGNMENT - 6


Encoders, Priority encoder and MUX

(T) Objective: 4 to 2, 8 to 3 and 16 to 4 encoders.

Software used: Logisim.

(A) 4 to 2 Encoder -

Block diagram :

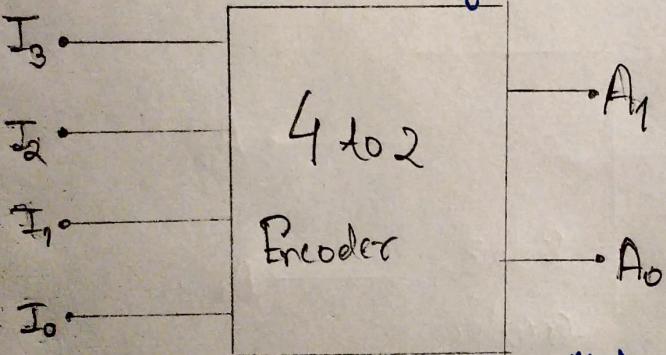

4 inputs give max^m of 2 outputs.
Opposite of decoders.

Truth table:


I_0	I_1	I_2	I_3	A_0	A_1
1	0	0	0	0	0
0	1	0	0	0	1
0	0	1	0	1	0
0	0	0	1	1	1

Expression:


Since A_0 is high
when I_2 is high or I_3
is high,

$$A_0 = I_2 + I_3$$


$$\text{Similarly, } A_1 = I_1 + I_3$$

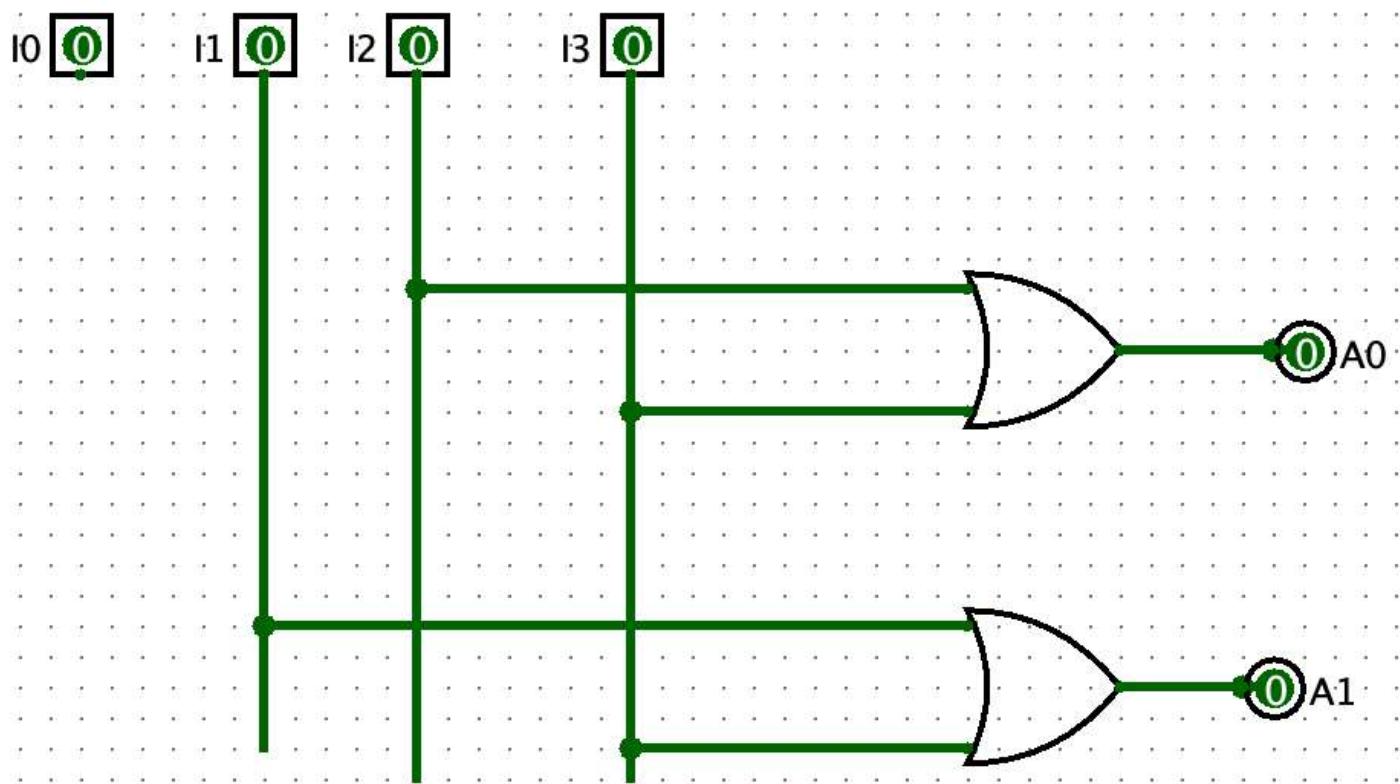

Circuit diagram:

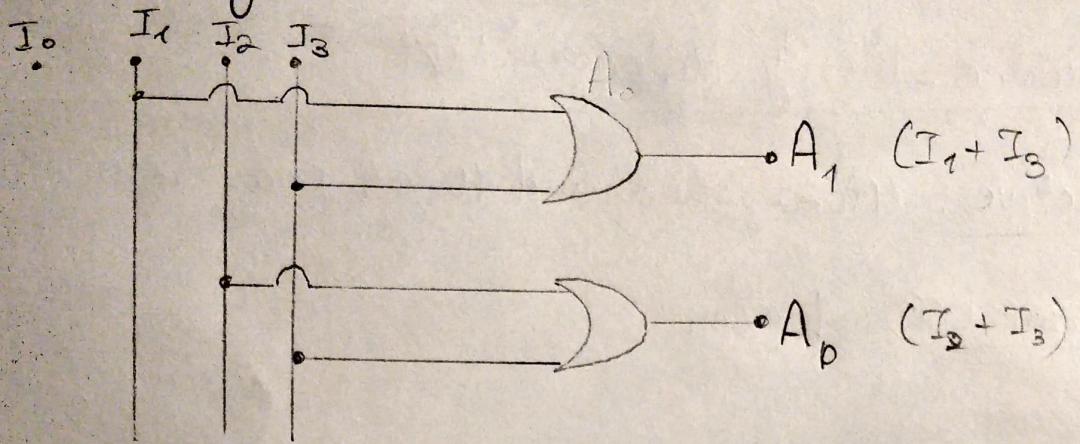

(B) 8 to 3 encoder —

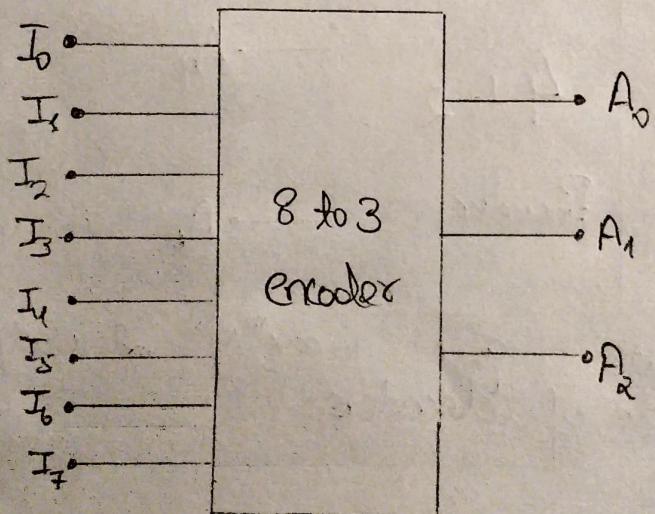

2^3 inputs give 3 outputs.

Truth table:


I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7	A_0	A_1	A_2
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1


Expression: $A_0 = I_4 + I_5 + I_6 + I_7$

$$A_1 = I_2 + I_3 + I_6 + I_7$$


$$A_2 = I_1 + I_3 + I_5 + I_7$$

Circuit diagram:

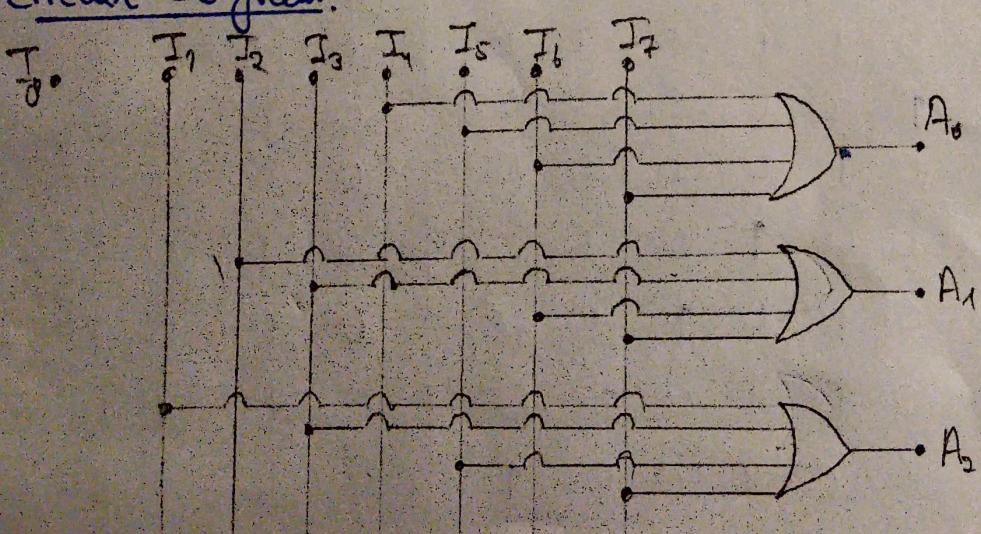

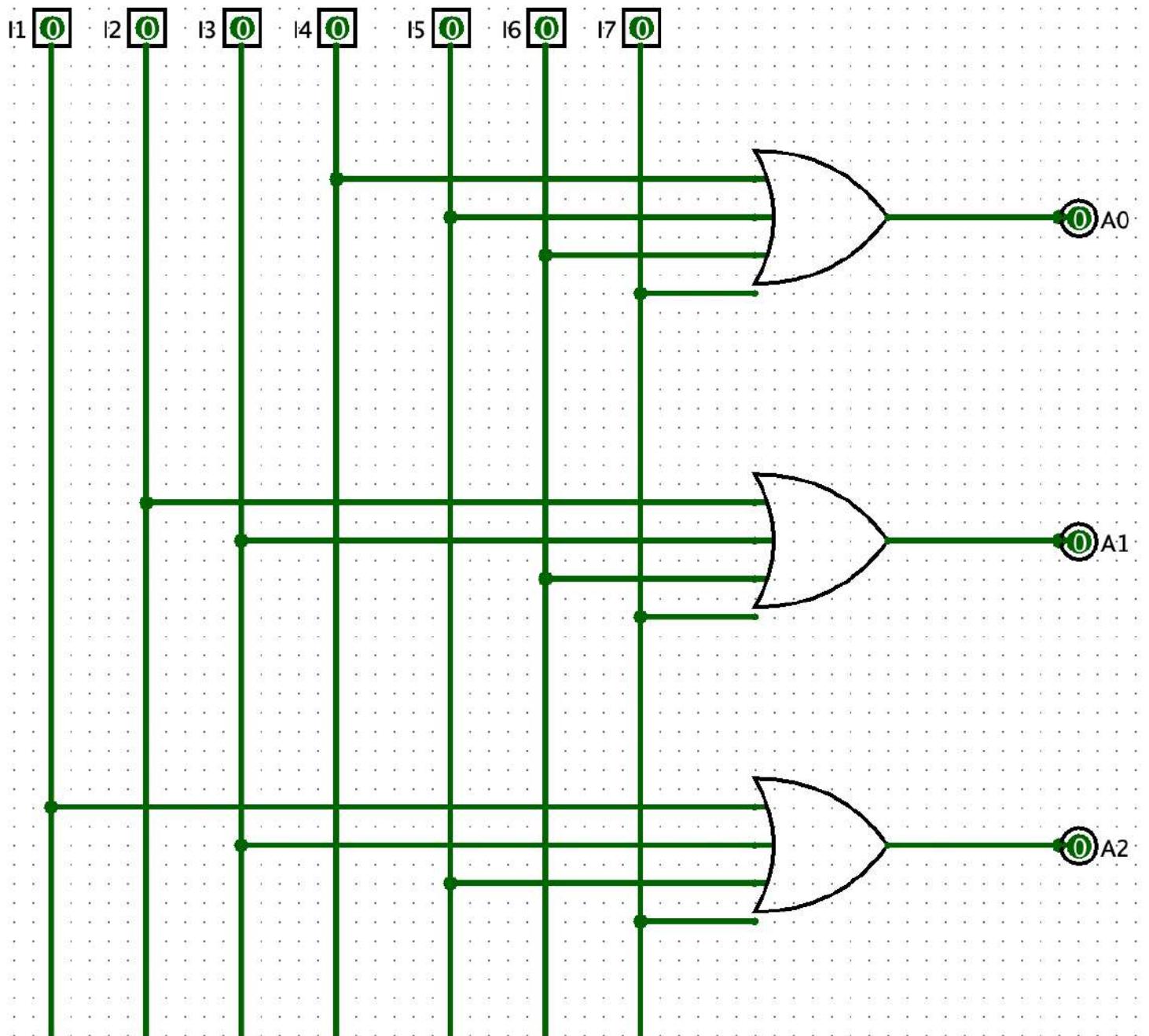

(C) 16 to 4 encoder —

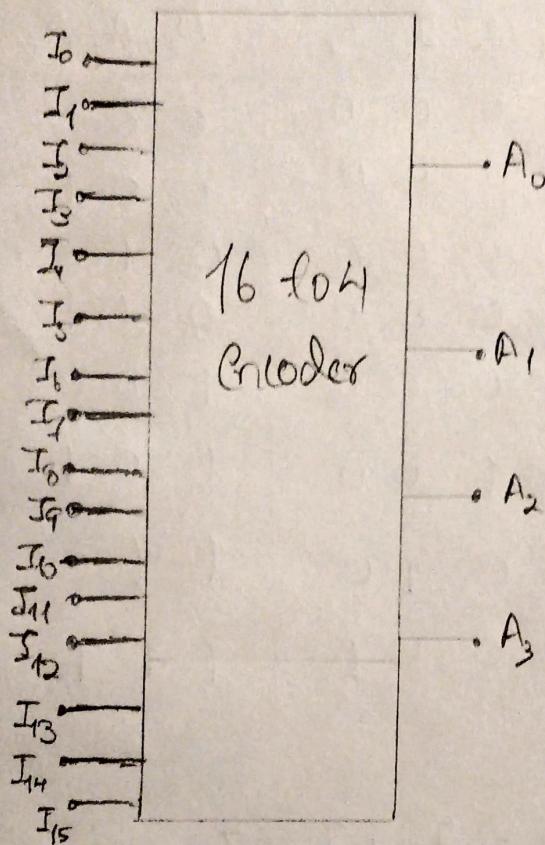

Truth table:

1st half:

I ₀	I ₁	I ₂	I ₃	I ₄	I ₅	I ₆	I ₇	A ₀	A ₁	A ₂	A ₃
1	0	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	0	1	0	0
0	0	0	0	0	1	0	0	0	1	0	1
0	0	0	0	0	0	1	0	0	1	1	0
0	0	0	0	0	0	0	1	0	1	1	1

2nd half:

I_8	I_9	I_{10}	I_{11}	I_{12}	I_{13}	I_{14}	I_{15}	A_0	A_1	A_2	A_3
1	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0	1	0	1	0
0	0	0	1	0	0	0	0	1	0	1	1
0	0	0	0	1	0	0	0	1	1	0	0
0	0	0	0	0	1	0	0	1	1	0	1
0	0	0	0	0	0	1	0	1	1	1	0
0	0	0	0	0	0	0	1	1	1	1	1


Expressions:

$$A_0 = I_8 + I_9 + I_{10} + I_{11} + I_{12} + I_{13} + I_{14} + I_{15}$$

$$A_1 = I_4 + I_5 + I_6 + I_7 + I_{12} + I_{13} + I_{14} + I_{15}$$

$$A_2 = I_2 + I_3 + I_6 + I_7 + I_{10} + I_{11} + I_{14} + I_{15}$$
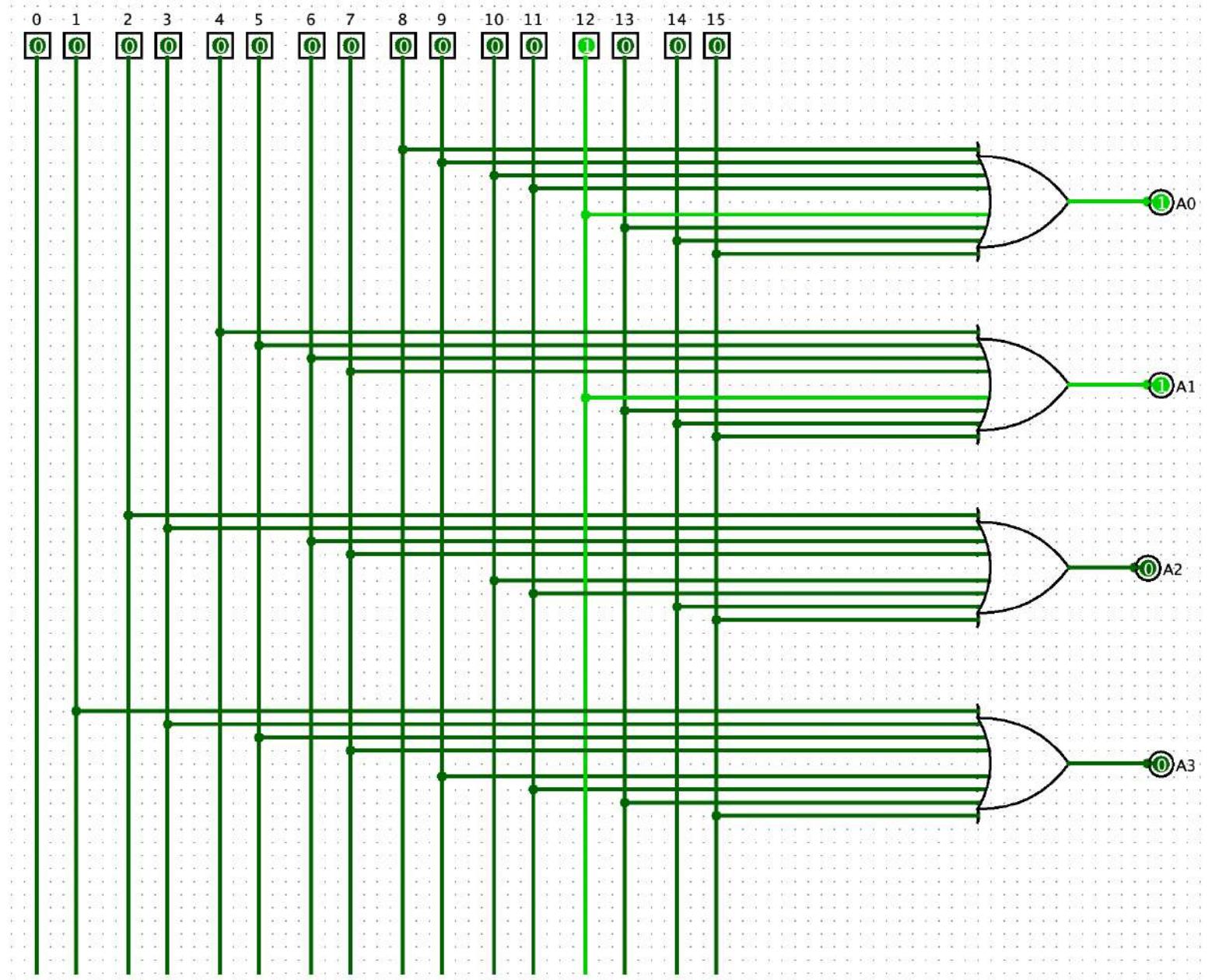
$$A_3 = I_1 + I_3 + I_5 + I_7 + I_9 + I_{11} + I_{13} + I_{15}$$




(II) Objective: 4 to 2 priority encoder

Software Used: Logisim

Theory:

Block Circuit diagram-

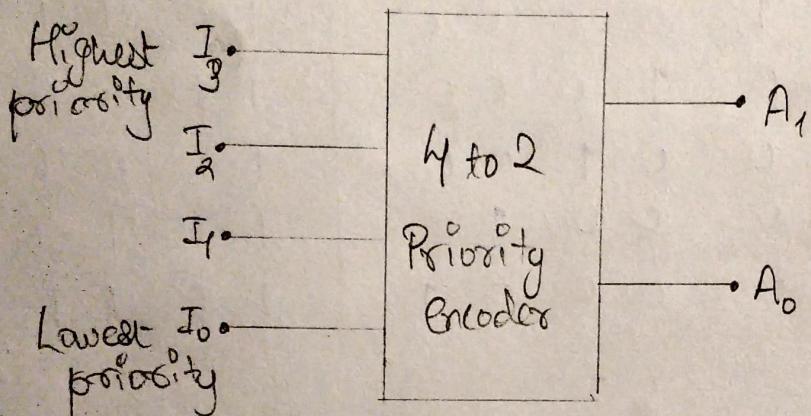

Truth table:

I ₀	I ₁	I ₂	I ₃	A ₀	A ₁
1	0	0	0	0	0
x	1	0	0	0	1
x	x	1	0	1	0
x	x	x	1	1	1

I_0	I_1	I_2	I_3	A_0	A_1	
0	0	0	0	x	x	(Undefined)
1	0	0	0	0	0	
x	[0 1 0 0]			0	1	
	[1 1 0 0]			0	1	
xx	[0 0 1 0]			1	0	
	[0 1 1 0]			1	0	
	[1 0 1 0]			1	0	
	[1 1 1 0]			1	0	
xxx	[0 0 0 1]			1	1	
	[0 0 1 1]			1	1	
	[0 1 0 1]			1	1	
	[0 1 1 1]			1	1	
	[1 0 0 1]			1	1	
	[1 0 1 1]			1	1	
	[1 1 0 1]			1	1	
	[1 1 1 1]			1	1	

Karnaugh:


$I_0 I_1$	$I_2 I_3$	00	01	11	10	A_o
00	x	1	1	1		
01		1	1	1		
11		1	1	1		
10		1	1	1		


$$\underline{A_o = I_3 + I_2}$$

$I_0 I_1$	$I_2 I_3$	00	01	11	10	A_o
00	x	1	1			
01		1	1			
11		1	1	1		
10		1	1			

$$\underline{A_o = I_1 I_2' + I_3}$$

Circuit diagram:

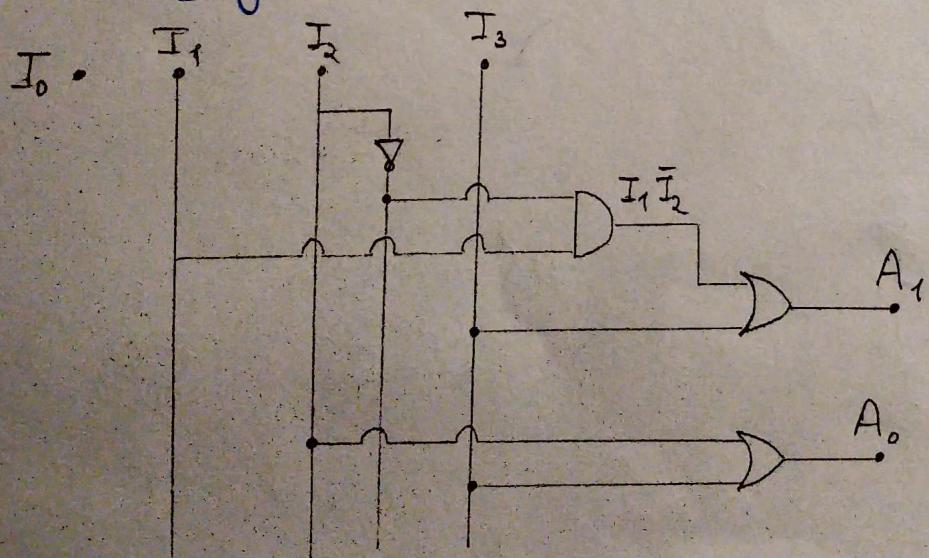

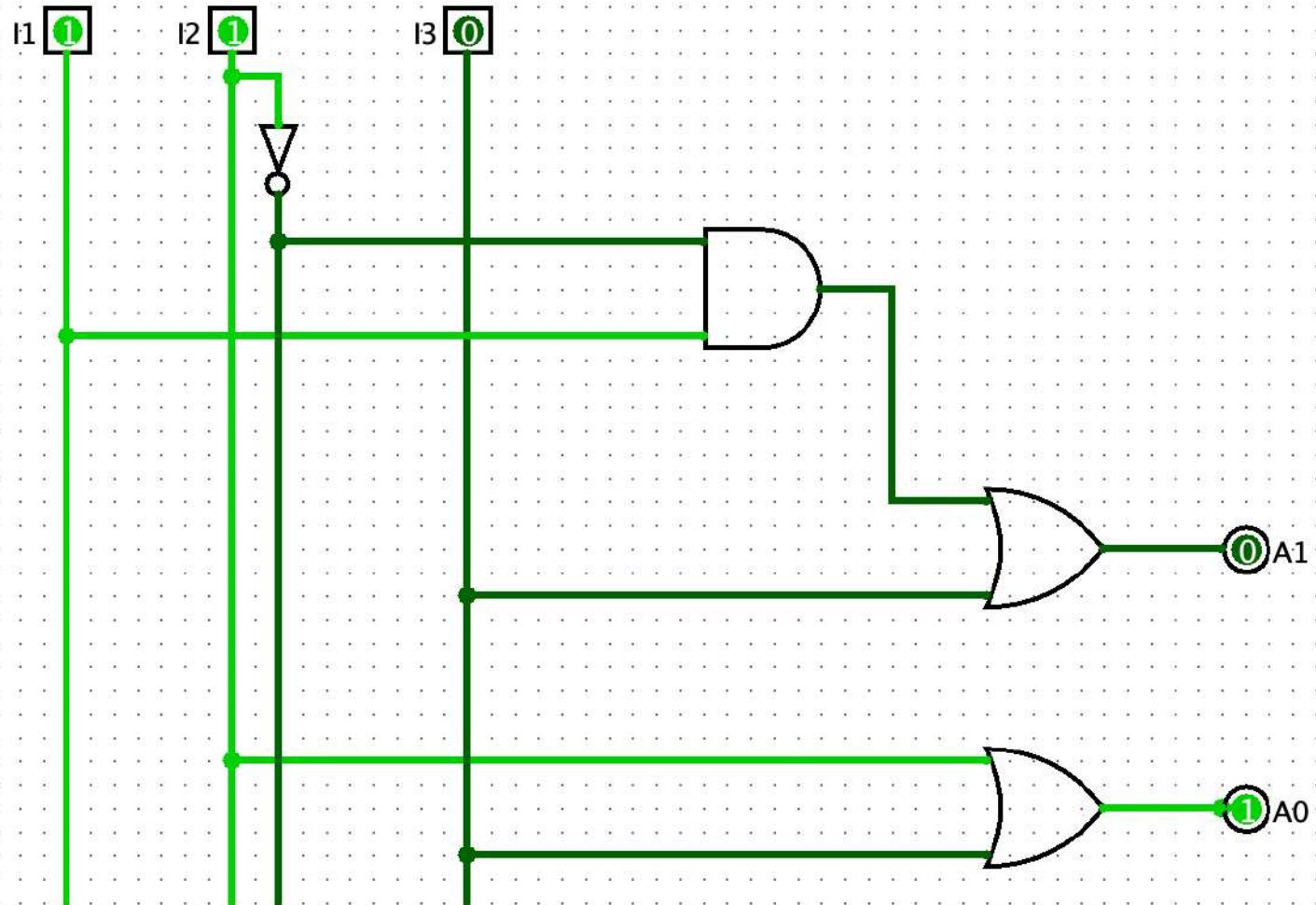


(II) Objective: 4×1 , 8×1 and 16×1 multiplexers.

Software used: Logisim

(A) 4×1 multiplexer:

Block diagram:

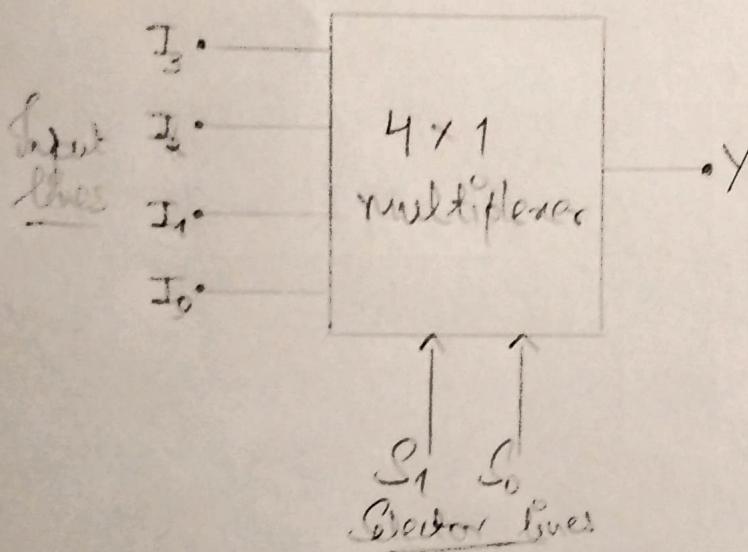


Truth table:


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Expression:

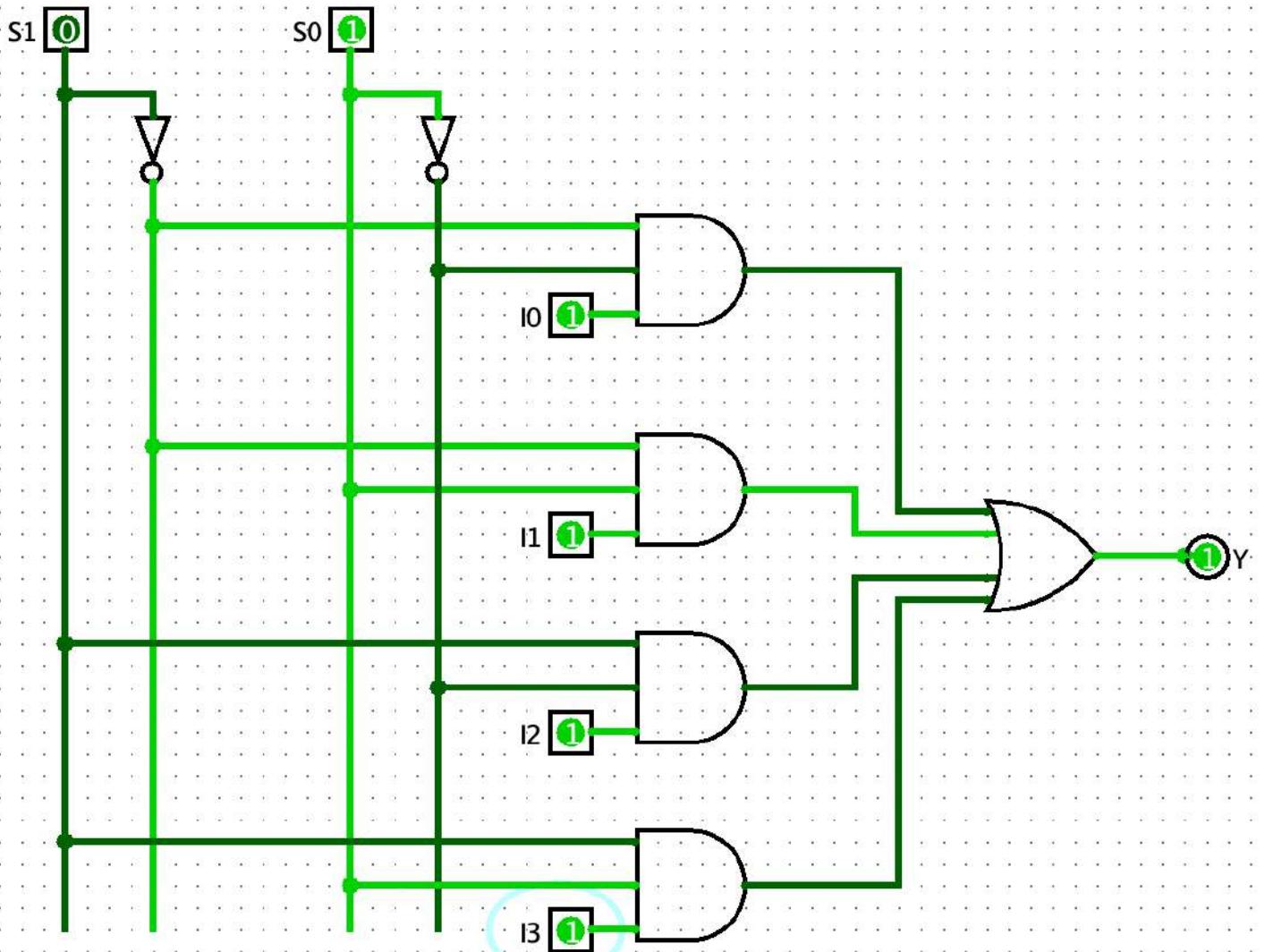
$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$



Circuit diagram:

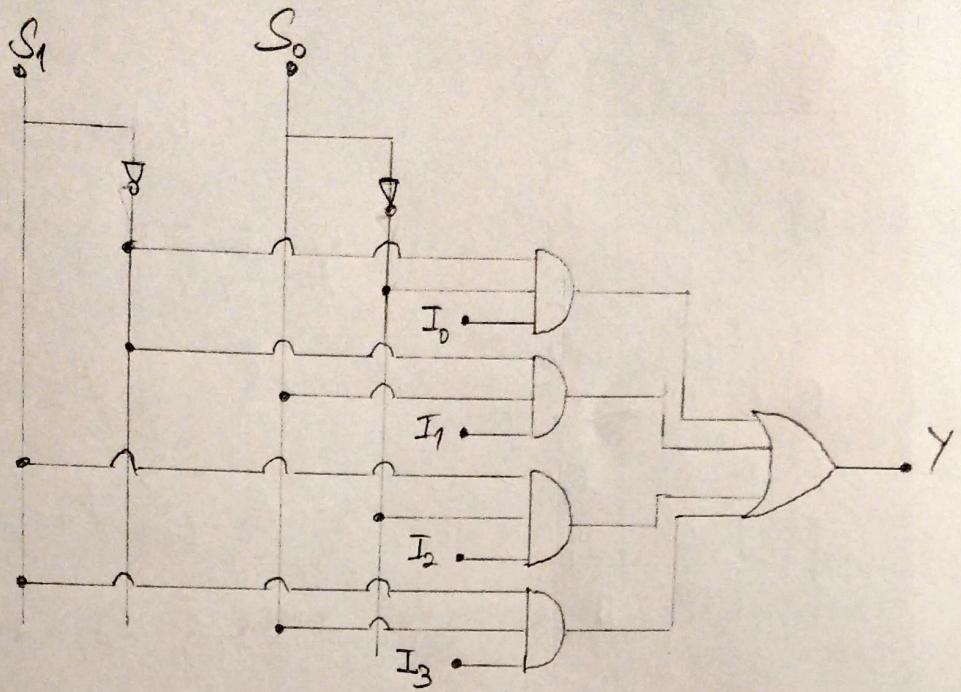

(B) 8×1 multiplexer:

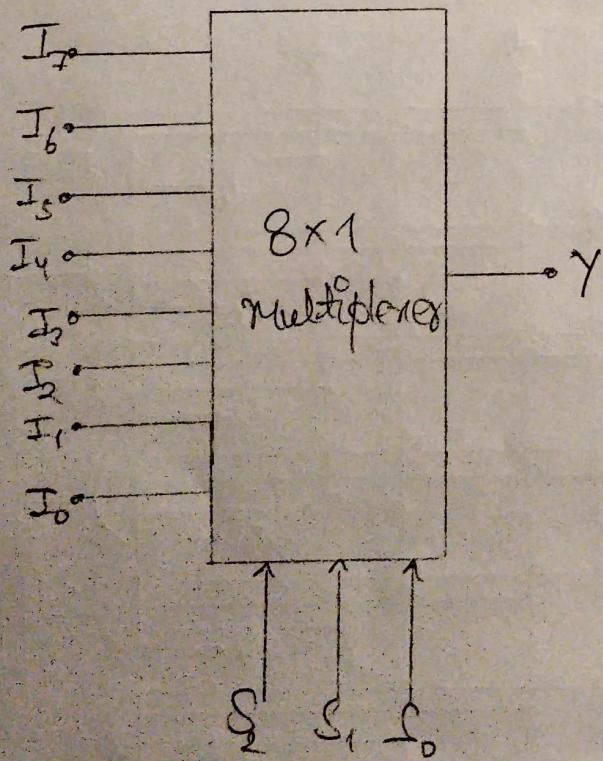


Truth table:


S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7

Expression:

$$\begin{aligned}
 Y = & \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 \\
 & + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 \\
 & + S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 \\
 & + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7
 \end{aligned}$$


Circuit diagram:

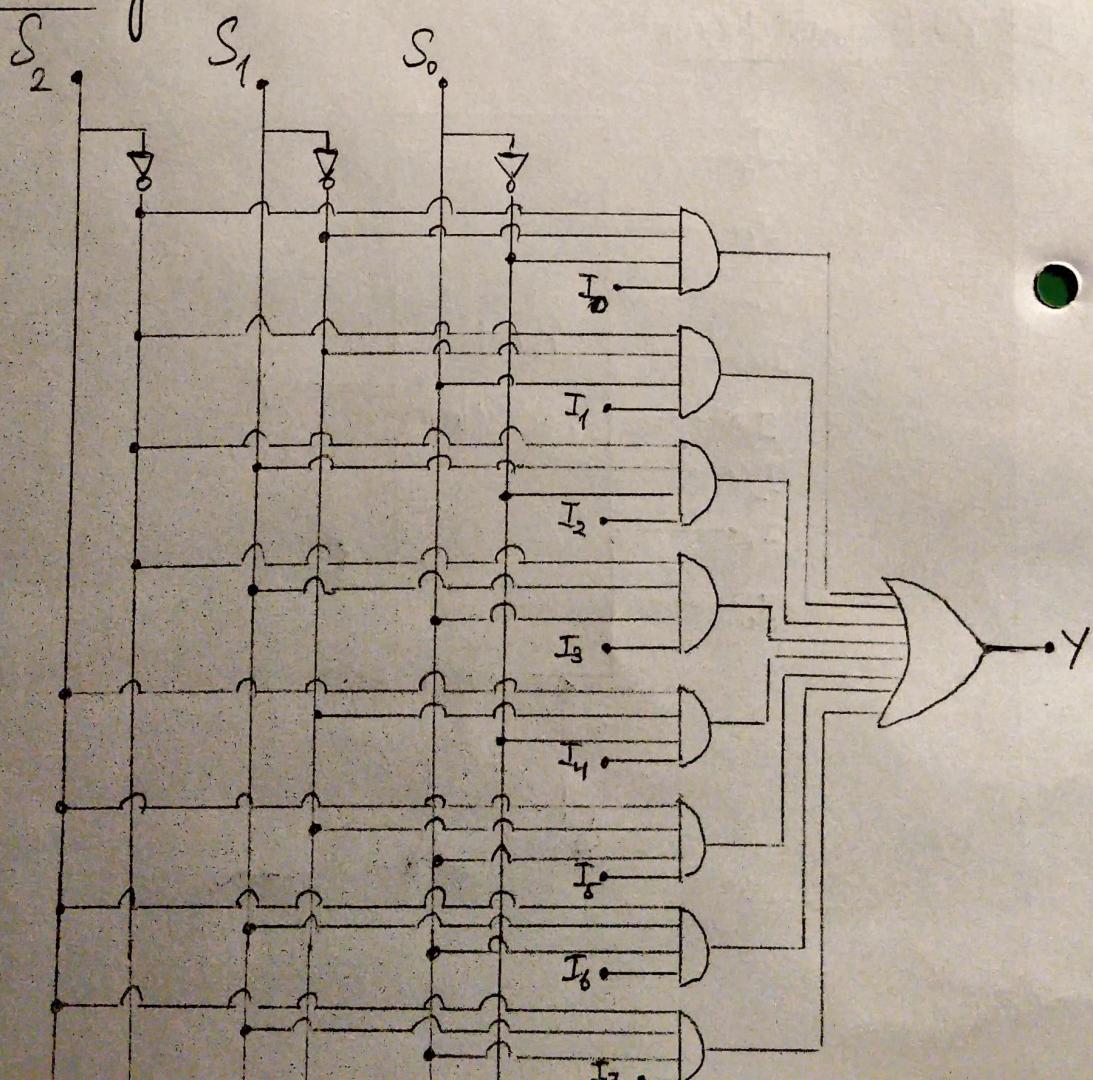

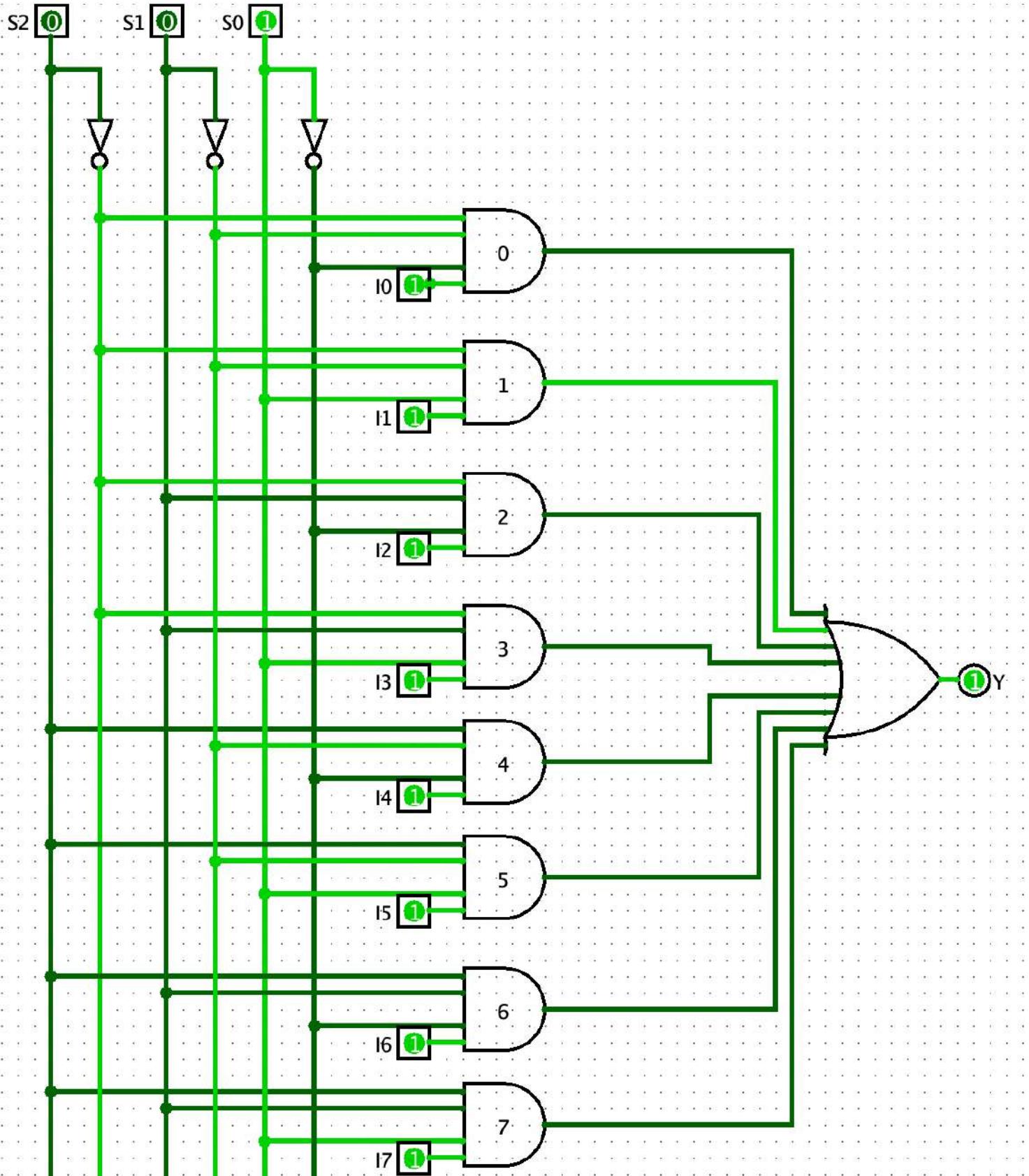

(Q) 16×1 multiplexer :

Block diagram:

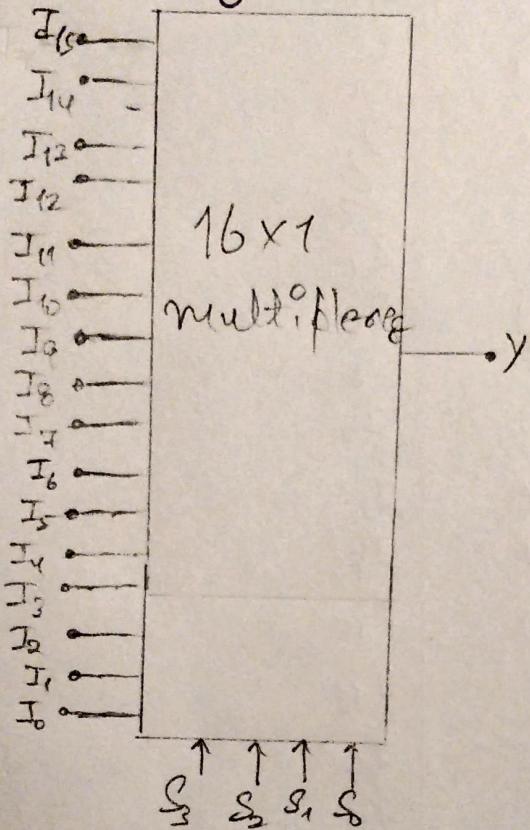

Truth table:

S_3	S_2	S_1	S_0	Y
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7
1	0	0	0	I_8
1	0	0	1	I_9
1	0	1	0	I_{10}
1	0	1	1	I_{11}
1	1	0	0	I_{12}
1	1	0	1	I_{13}

Truth table:

S_3	S_2	S_1	S_0	Y
0	0	0	0	I_0
0	0	0	1	I_1
0	0	1	0	I_2
0	0	1	1	I_3
0	1	0	0	I_4
0	1	0	1	I_5
0	1	1	0	I_6
0	1	1	1	I_7
1	0	0	0	I_8
1	0	0	1	I_9
1	0	1	0	I_{10}
1	0	1	1	I_{11}
1	1	0	0	I_{12}
1	1	0	1	I_{13}
1	1	1	0	I_{14}
1	1	1	1	I_{15}

Expression:

$$\begin{aligned}
 Y = & \bar{S}_3 \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_3 \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_3 \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_3 S_2 S_1 \bar{S}_0 I_3 \\
 & + \bar{S}_3 S_2 \bar{S}_1 \bar{S}_0 I_4 + \bar{S}_3 S_2 \bar{S}_1 S_0 I_5 + \bar{S}_3 \bar{S}_2 S_1 \bar{S}_0 I_6 + \bar{S}_3 \bar{S}_2 S_1 S_0 I_7 \\
 & + S_3 \bar{S}_2 \bar{S}_1 \bar{S}_0 I_8 + S_3 \bar{S}_2 \bar{S}_1 S_0 I_9 + S_3 \bar{S}_2 S_1 \bar{S}_0 I_{10} + S_3 \bar{S}_2 S_1 S_0 I_{11} \\
 & + S_3 \bar{S}_2 \bar{S}_1 \bar{S}_0 I_{12} + S_3 \bar{S}_2 \bar{S}_1 S_0 I_{13} + S_3 S_2 S_1 \bar{S}_0 I_{14} + S_3 S_2 S_1 S_0 I_{15}
 \end{aligned}$$

