

Date: 18/3/22

Submitted by → (See B)
Anushthan Saxena
Seo210010027

LAB REPORT-12

Programmable 1-bit ALU

Aim: To design a 1 bit ALU using the given function table.

Software used: Logisim


Provided table:

F_2	F_1	F_0	ALU function	Y_1	Y_0
0	0	0	Zero (0)	-	0
0	0	1	A OR B	-	A+B
0	1	0	A AND B	-	A.B
0	1	1	A XOR B	-	$A \oplus B$
1	0	0	A PLUS B	Carry	Sum
1	0	1	A MINUS B	Borrow	Difference
1	1	0	A PLUS B PLUS C	Carry	Sum
1	1	1	A MINUS B MINUS C	Borrow	Difference

Theory →

- First 4 functions are logical and generate 1 bit output.
- Last 4 functions give 2 bit outputs, are arithmetic functions.

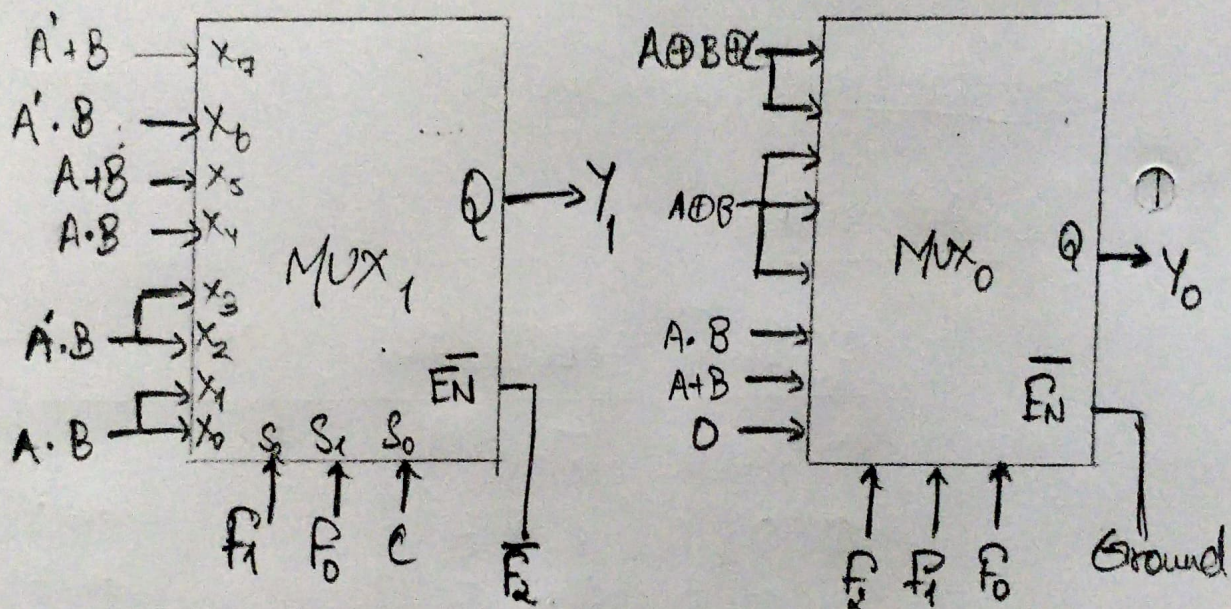→ The final ALU output is generated using 2 8-bit MUXs: MUX₀ for Y_0 and MUX₁ for Y_1 . The required inputs and outputs are mentioned below. MUX₀ is always enabled.



→ The inputs $A.B$, $A'.B$, $A+B$ and $A'+B$ can be generated using 4 2-bit MUXs.

