

Date: 8/1/22

Submitted by -

1

ASSIGNMENT - 2


S2021 001 0027

Anushthana Saxena

(Sec B)

$$\begin{aligned}
 Q1 Q) F &= a'b'c + ab'c + abc' + abc \\
 &= a'b'c + abc + ab'c + abc' \\
 &= b'c(a+a') + a(b'c + bc') \\
 &= b'c + a(b \oplus c)
 \end{aligned}$$

Since
 $(a+a'=1)$

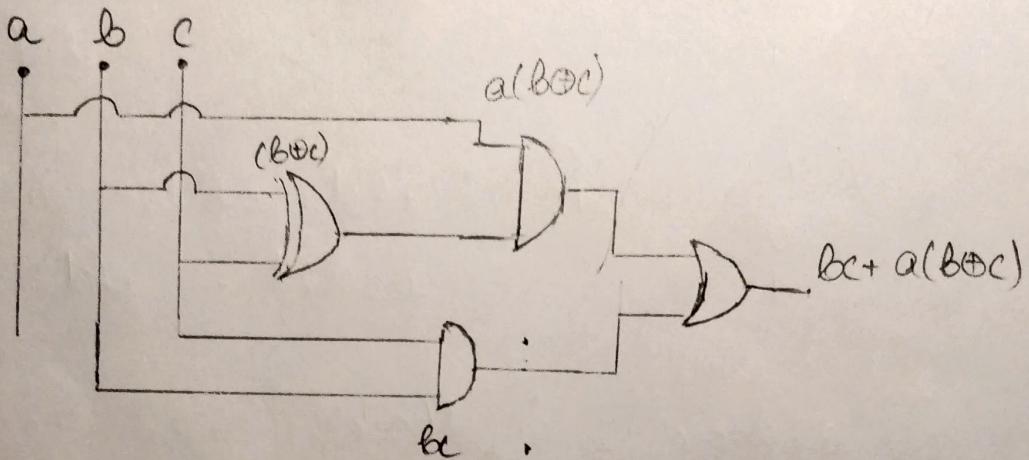

$$Q2) F = (\bar{a}\bar{b} + \bar{a}c + \bar{a}b + ac)'$$


$$= (\bar{a}\bar{b} + \bar{a}b + \bar{a}c + ac)'$$

$$= (\bar{a}(b+\bar{b}) + c(a+\bar{a}))' \quad (x+x=1)$$

$$= (\bar{a} + c)'$$

$$= ac'$$

By DeMorgan's law

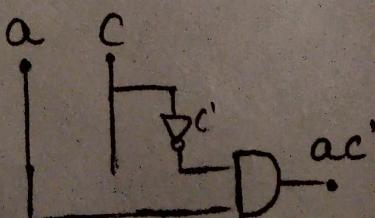

$$Q_2 \quad f = a'd + b'd + bd$$

$$f = a'd(b+b') + b'd(a+a') + bd(a+a')$$

$$= \underline{a'b'd} + \underline{a'b'd} + ab'd + \underline{a'b'd} + abd + \underline{a'b'd}$$

$$f = a'b'd + a'b'd + ab'd + abd \quad (\text{since } \cancel{a'b'd} + \cancel{a'b'd} = \cancel{a'b'd})$$

$$f = a'b'd(c+c') + a'b'd(c+c') + ab'd(c+c') + abd(c+c')$$

$$f = a'b'cd + a'b'c'd + a'b'cd + a'b'c'd$$

$$+ ab'cd + ab'c'd + ab'cd + abc'd$$

$$\Rightarrow f = \Sigma(7, 8, 5, 3, 1, 13, 9, 15, 11) \Rightarrow f = \underline{\Sigma(1, 3, 5, 7, 9, 13, 15)}$$

$$\Rightarrow f = \pi(0, 2, 4, 6, 8, 10, 12, 14)$$

$$(f' = \Sigma(0, 2, 4, 6, 8, 10, 12, 14) = \pi(1, 3, 5, 7, 9, 11, 13, 15))$$

$$f = a'b'cd + a'b'c'd + a'b'cd + a'b'c'd + ab'cd + abc'd + ab'cd + abc'd = \Sigma(1, 3, 5, 7, 9, 11, 13)$$

$$f' = (a'b'cd + a'b'c'd + a'b'cd + a'b'c'd + ab'cd + abc'd + ab'cd + abc'd)'$$

$$= (a'b'cd)' (a'b'c'd)' (a'b'cd)' (a'b'c'd)' \quad (\text{Following DeMorgan's law})$$

$$(ab'cd)' (ab'c'd)' (abc'd)' (ab'c'd)'$$

$$F' = \frac{(a+b+c+d')(a+b'+c+d')}{(a+b'+c+d)} \frac{(a+b'+c'+d')}{(a'+b'+c+d)} \frac{(a'+b'+c+d)}{(a'+b'+c+d')}$$


Q3 (a) $F(a, b, c) = \sum(1, 2, 6) = \pi(0, 3, 4, 5, 7)$
 $= \pi(0, 3, 5, 7)$

(b) $F(a, b, c, d) = \pi(3, 6, 7, 11) = \sum(0, 1, 2, 4, 5, 8, 9, 10, 12, 13, 14, 15)$

Q4 $y_1 = a \oplus (c+d+e), \quad y_L = [f(c+d+e)b']'$
 $= f b' (c+d+e)$

Q5 $F = xy + y'z + x'y'$

i) Use AND, OR and Inverter

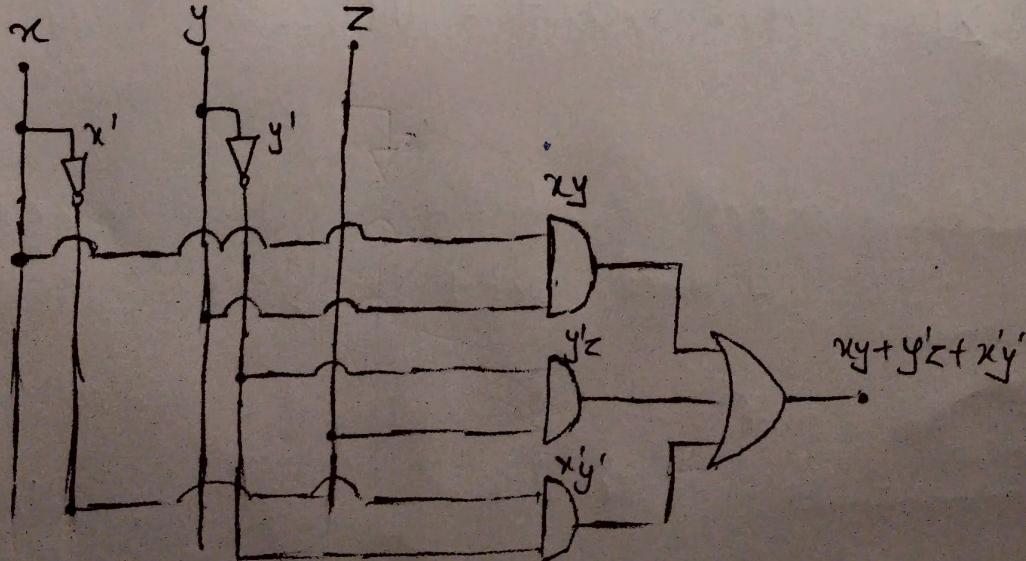

b) With OR and Inverter gates

$$F = xy + x'y' + y'z$$

$$= (x'+y')' + (x')' + (y')' + (z')'$$

$$= x + x' + y + y' + z + z'$$

$$= y + z' [(xy + x'y' + y'z)']$$

$$= (x'y'z)^{'}$$


DeMorgan's
 $(ab)' = (a'+b')'$

Since
 $(a+a'=1)$
 and $(1+a=1)$

b) With OR and Inverter gates


$$F = xy + x'y' + y'z = (x'+y')' + (x+y)' + (y+z)'$$

(DeMorgan)
 law

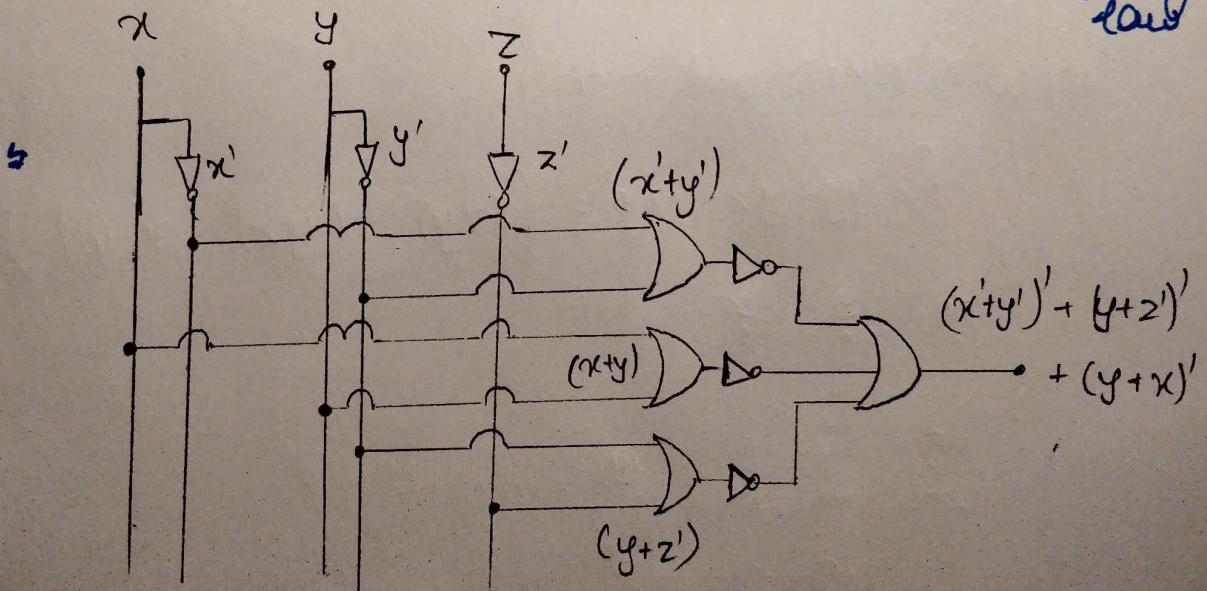

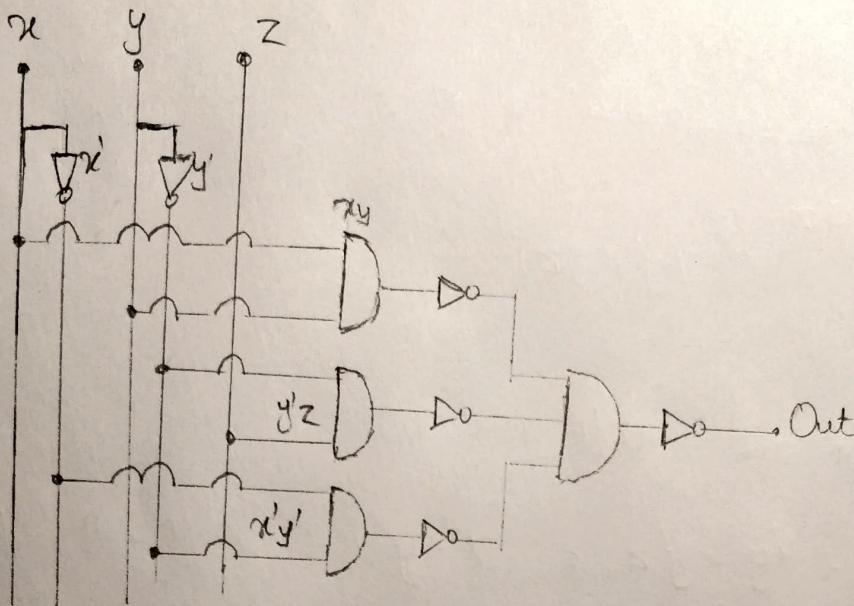c) With AND and inverter


$$F = xy + y'z + x'y' = ((xy)' (y'z)' (x'y')')'$$



(DeMorgan's law)

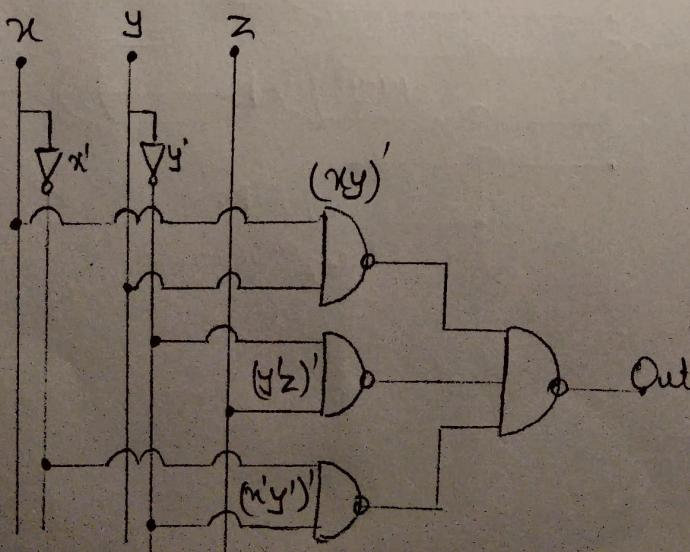d) With NAND and inverter


$$F = xy + y'z + x'y' = ((xy)' (y'z)' (x'y')')'$$



(e) With NOR and inverter gates.

$$F = xy + x'y' + y'z = (x+y')' + (x+y) + (y+z')'$$

(By DeMorgan's law)

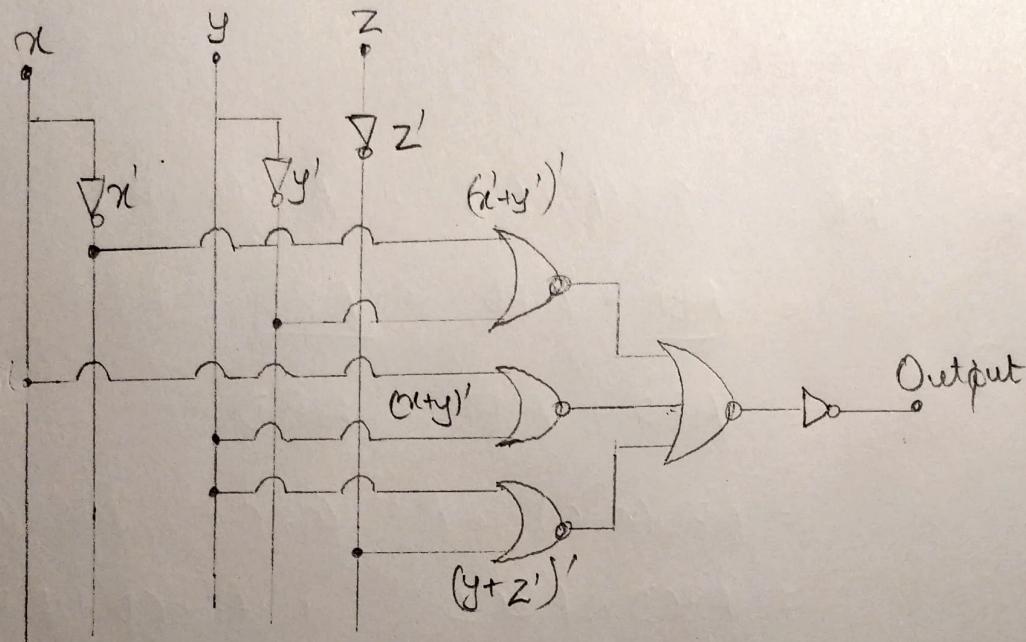

Q6 Show AND followed by inverter and inverter followed by OR are ~~the same~~ same.

$\Rightarrow \text{TP: } (AB)' = \overline{(A'+B')}$

Or $\text{TP: } AB + (A'+B') = 1$ And (ii) $AB(A'+B') = 0$

$\text{Q) LHS: } AB + (A'+B') = (A'+B+A)(A'+B+B)$
 $= (1+B')(1+A')$
 $= 1 \cdot 1 = 1 = \text{RHS}$

Proved

$$\begin{aligned} & [x+a+b \\ & = (x+a)(a+b)] \\ & [1+x=x] \end{aligned}$$

$$(ii) LHS = AB(A'+B') = AA'B + ABB' \\ = 0 + 0 = 0$$

$[xx' = 0]$

Therefore $(AB)' = (A'+B')$ proved

Q7 $F(A, B, C, D) = \underline{BD} + AD + \underline{BD}$

$$\begin{aligned} f = BD + AD &= BD(A+A') + AD(B+B') \\ &= \underline{ABD} + A'\underline{BD} + \underline{ABD} + AB'D \\ &= ABD + A'BD + AB'D \\ &= ABD(C+C') + A'BD(C+C') + AB'D(C+C') \\ &= ABCD + ABC'D + A'BCD + A'BC'D \\ &\quad + AB'C'D + AB'C'D \end{aligned}$$

$$\Rightarrow F = \sum(15, 13, 7, 5, 11, 9) \equiv \sum(5, 7, 9, 11, 13)$$

$$\Rightarrow F = \sum(0, 1, 2, 3, 4, 6, 8, 10, 12, 14)$$

$$\begin{aligned} &= (A+B+C+D)(A+\bar{B}+C+\bar{D})(A+B+\bar{C}+D)(A+B+\bar{C}+\bar{D}) \\ &\quad (\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+\bar{C}+D) \\ &\quad (\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+\bar{B}+\bar{C}+D) \end{aligned}$$

Q8 (a) $F = xy + xy' + y'z$

Truth table:

$$\begin{aligned} F &= x(y+y') + y'z \\ &= x + y'z \end{aligned}$$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

(b) $F = bc + Q'C'$

Truth table:

a	b	c	bc	$Q'C'$	F
0	0	0	0	1	1
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	1	0	1