

1


Date: 12/3/22

LAB REPORT - 11Submitted by → (Sec B)
S2021 001 0027
Anushthan Saxena


Ring Counter, Johnson's counter, Modulo N

AIM → Implementation of 5 bit ring counter, 5 bit Johnson counter and examples of Modulo N counters.SOFTWARE USED → Logisim(I) 5 bit Ring Counter →

Clock input	Q_4	Q_3	Q_2	Q_1	Q_0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	1	0	0
4	0	1	0	0	0
5	Φ	0	0	0	0
6	0	0	0	0	1
7	0	0	0	1	0
8	0	0	1	0	0
9	0	1	0	0	0
10	1	0	0	0	0

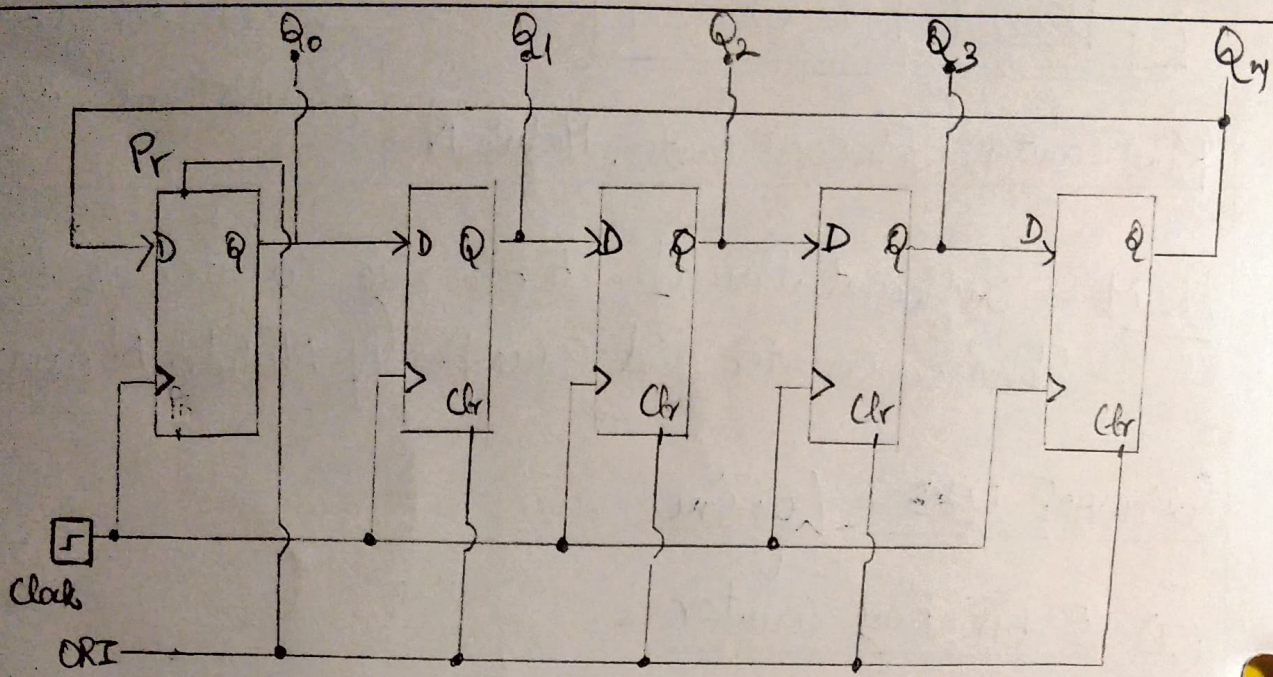


5 bit ring counter using D flip flops

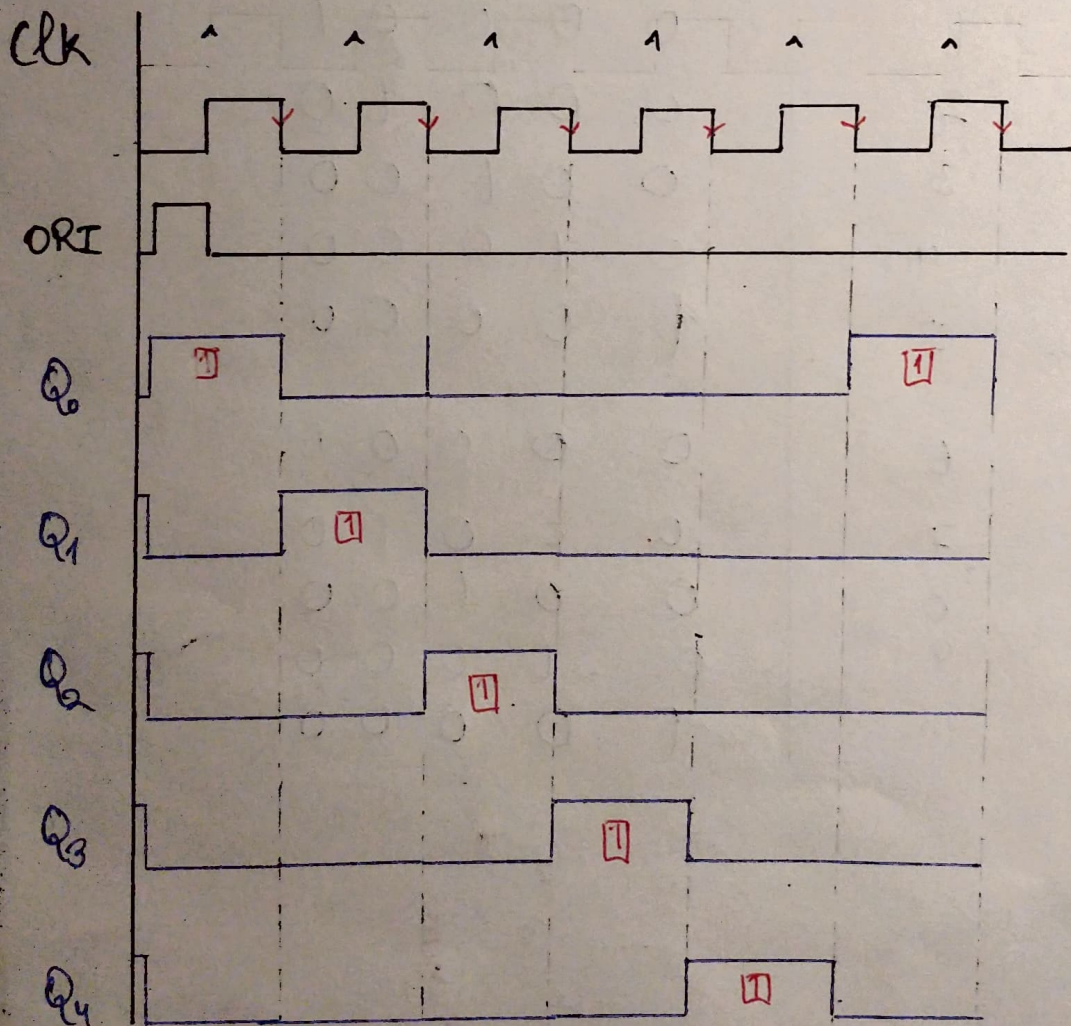


(II) 5 bit Johnson Counter →


Clock input	Q_4	Q_3	Q_2	Q_1	Q_0
1	0	0	0	0	0
2	0	0	0	0	1
3	0	0	0	1	1
4	0	0	1	1	1
5	0	1	1	1	1
6	1	1	1	1	1
7	1	1	1	1	0
8	1	1	1	0	0
9	1	1	0	0	0
10	1	0	0	0	0
	0	0	0	0	0

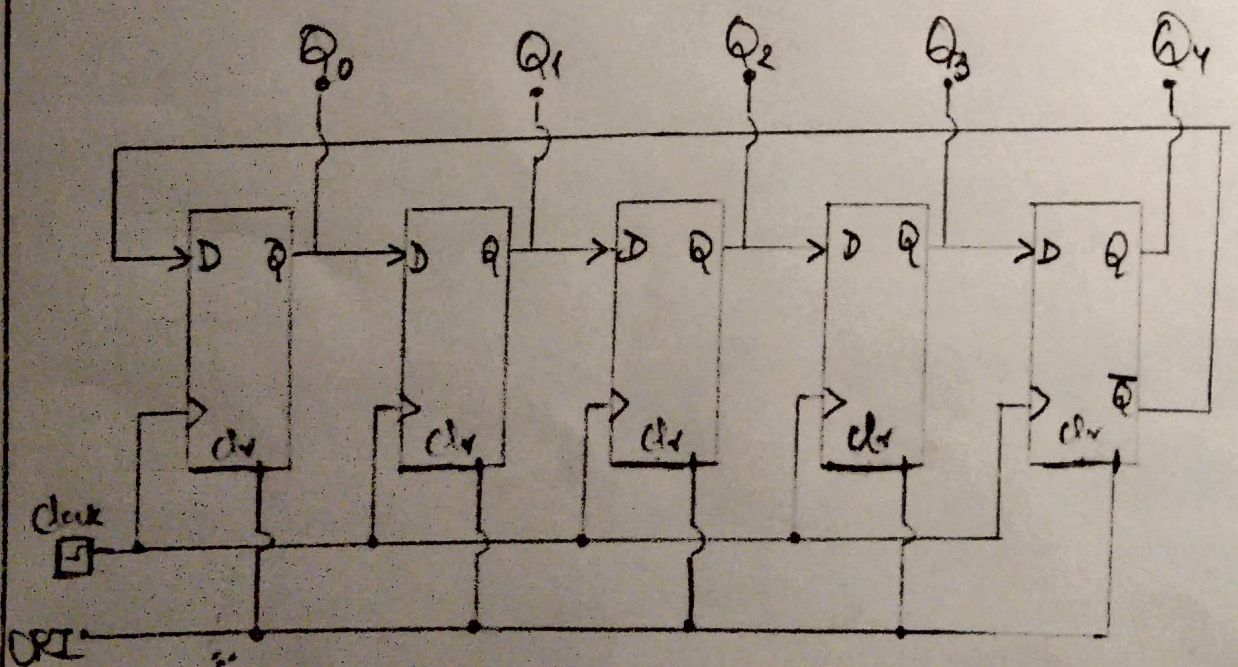


4

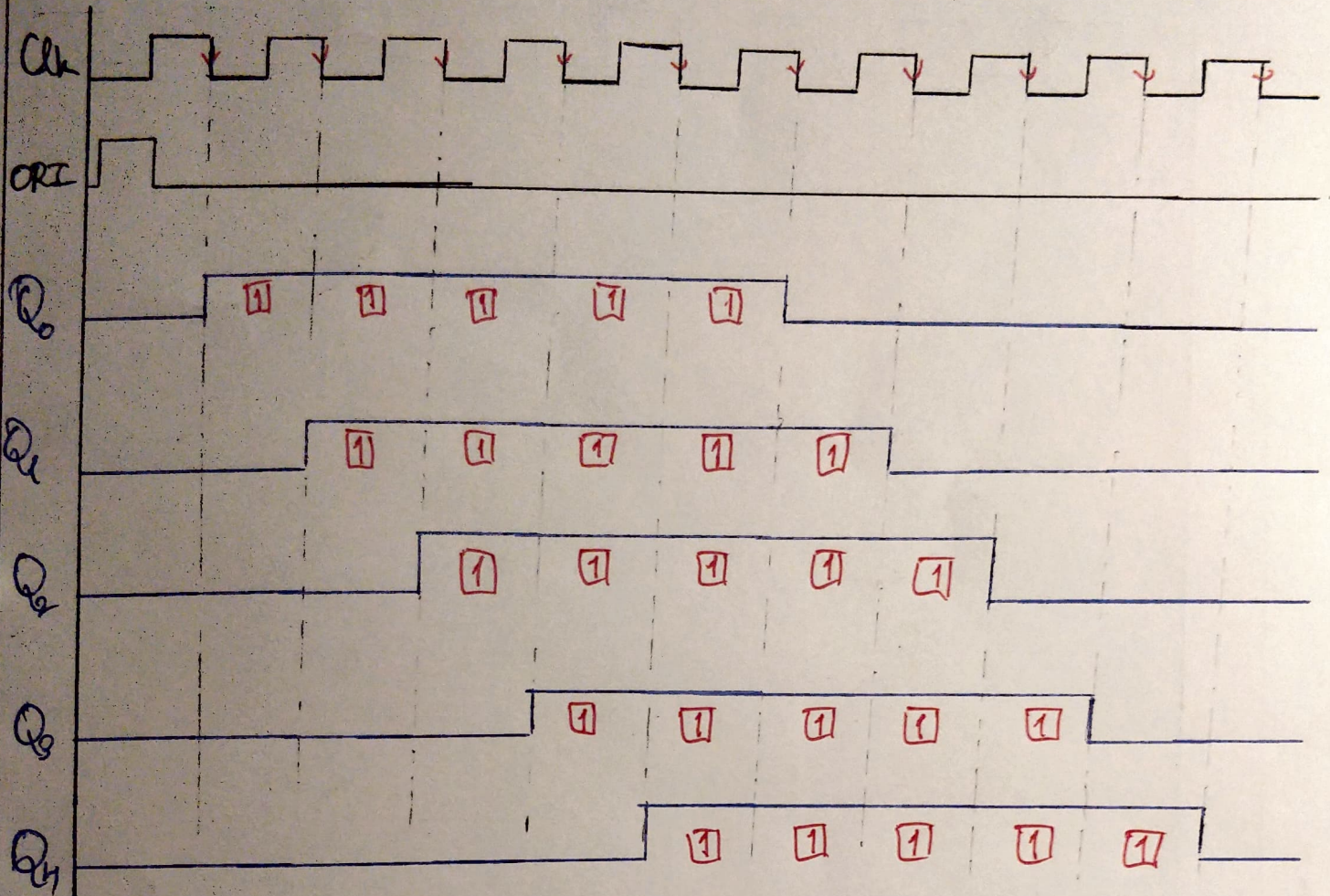

Ring counter

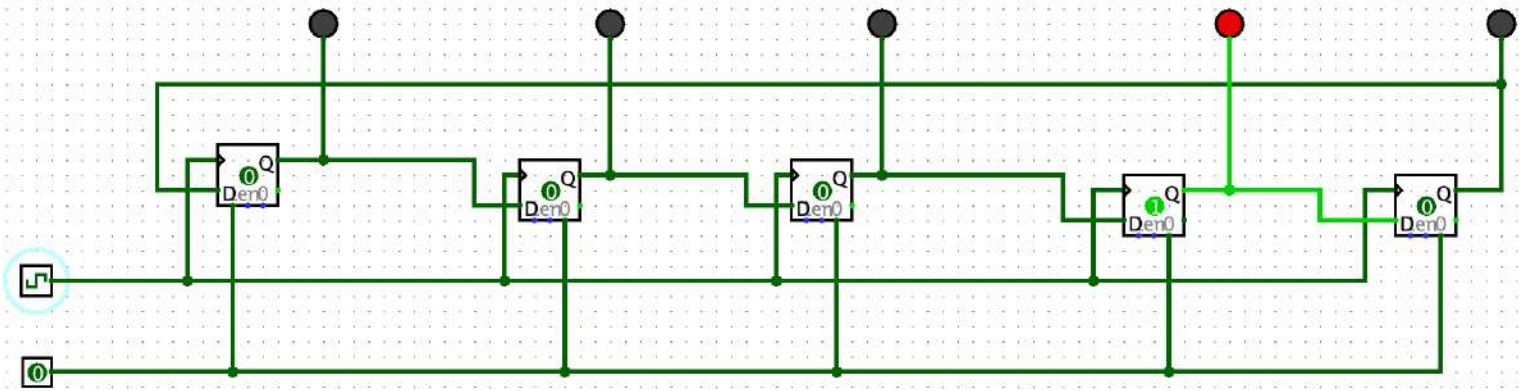


Johnson's counter

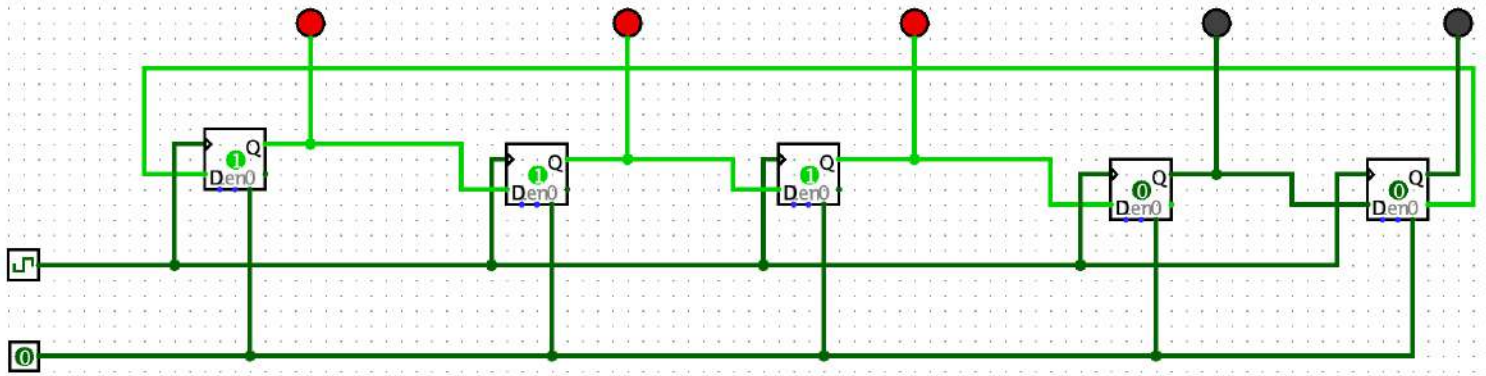


(III) 1-6 Counter →

Present state			Next-state		
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	0	0	1

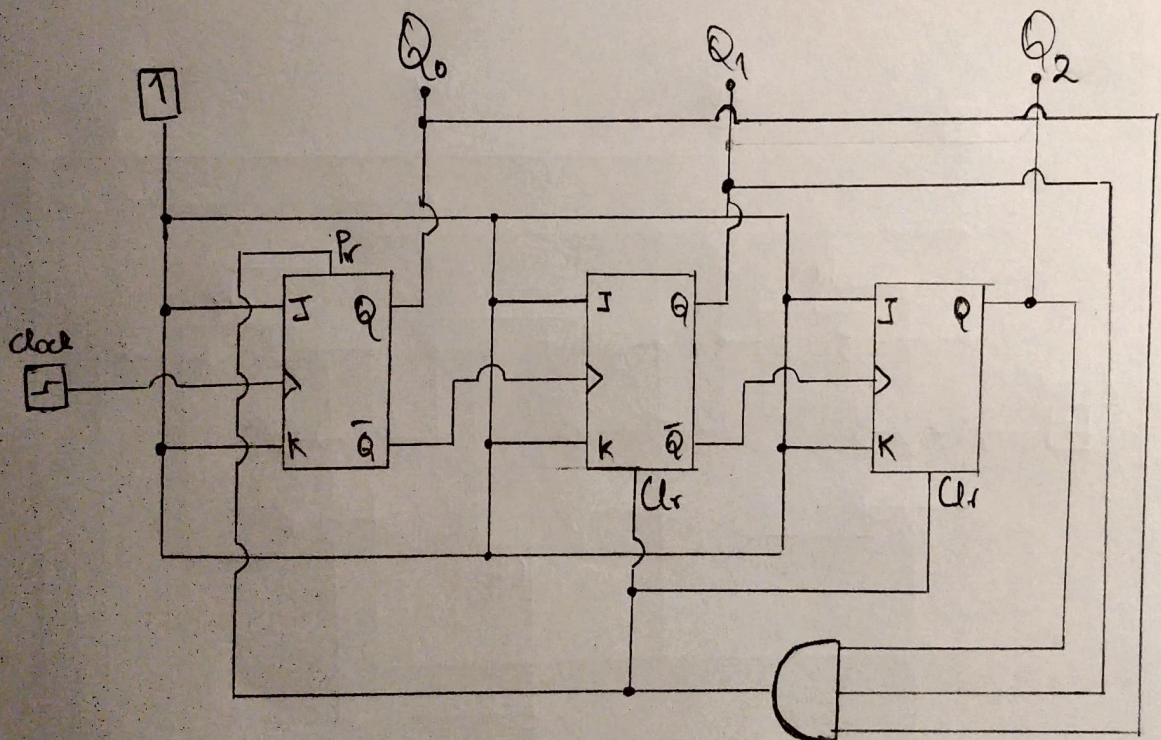


(TV) 5-2 down counter →

Present state			Next state		
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+
1	0	1	1	0	0
1	0	0	0	1	1
0	1	1	0	1	0
0	1	0	1	0	1

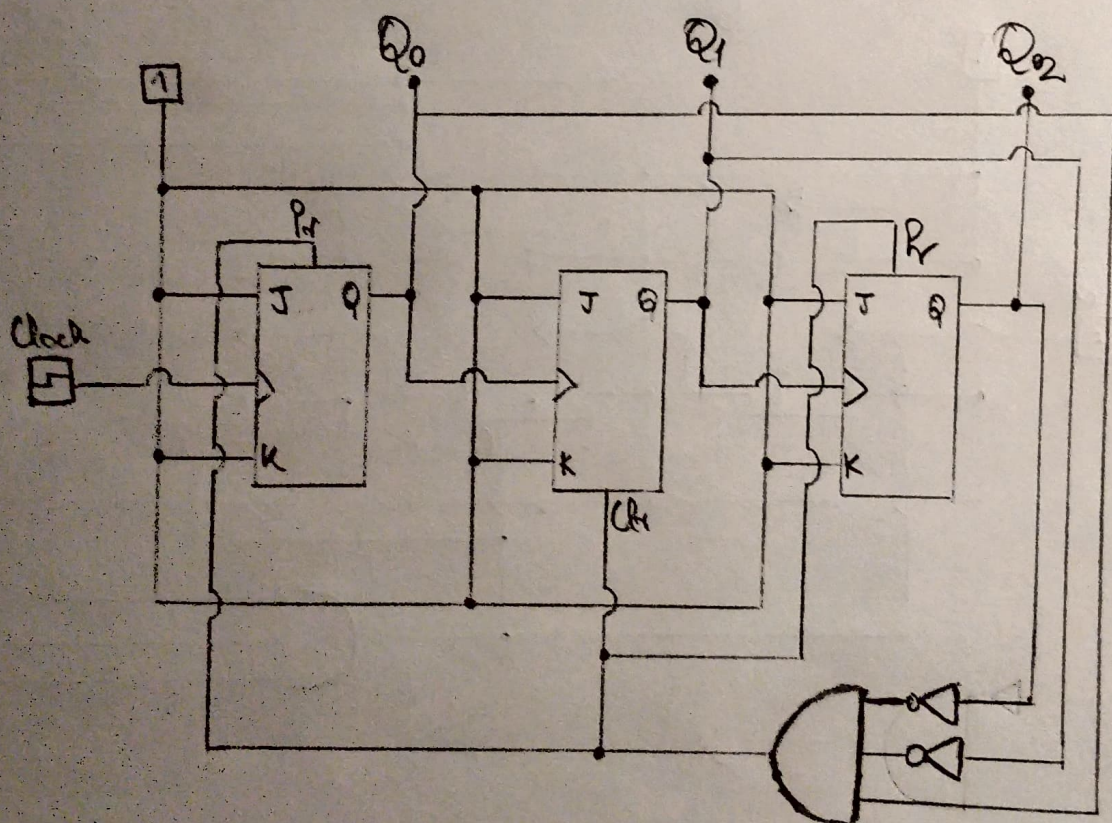

1-6 Counter

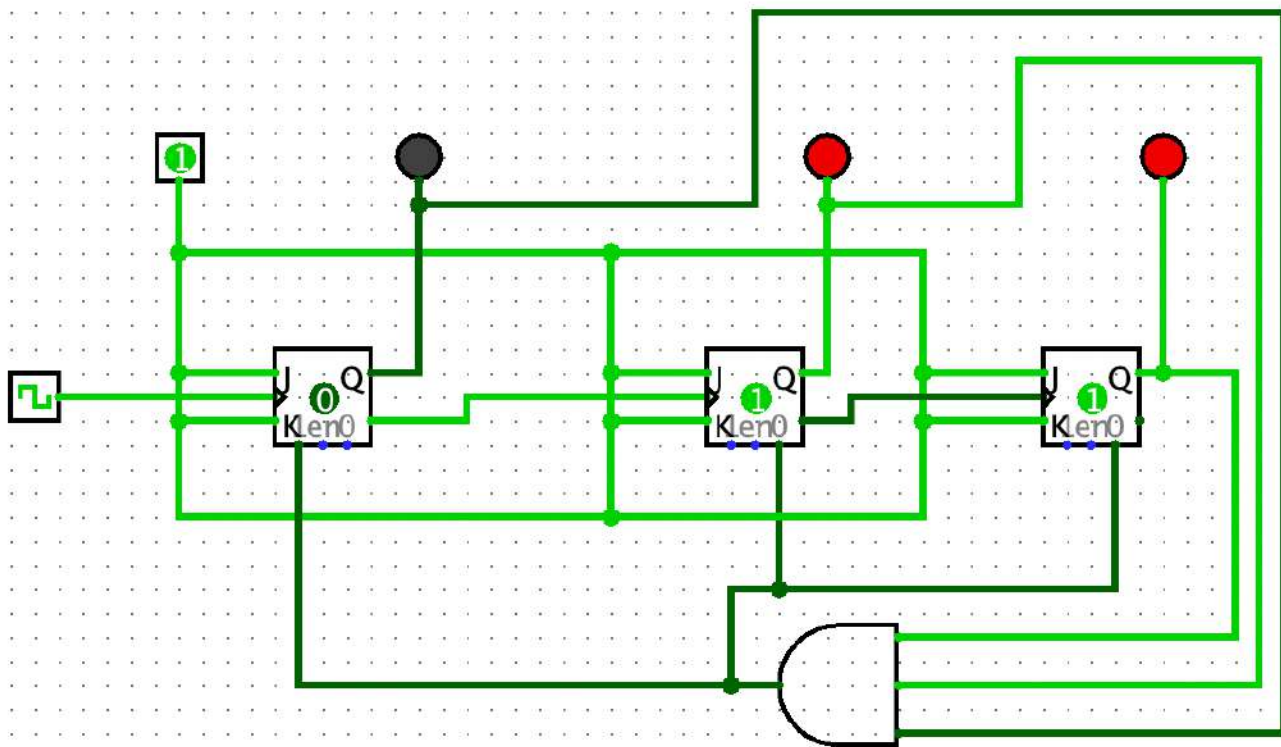

5-2 counter

